



SPICE (A007)

國研院國家晶片系統設計中心

July. 2005

王朝琴 Email: hotline@cic.org.tw



Course Objectives

- Know **Basic elements for circuit simulation**
- Learn the **basic usage of standalone spice simulators**
- Know the **concept of device models**
- Learn the **usage of waveform tools**
- **Advanced features of spice simulator**



Further Reading

- **HSPICE 使用手冊**
PDF格式檔：`/usr/meta/cur/docs/pdf/2001.4_hspice.pdf`
- **HSPICE 版本新增功能說明**
PDF格式檔：`/usr/meta/cur/docs/pdf/2001.4_release_notes.pdf`
- **HSPICE - awaves 使用手冊**
PDF格式檔：`/usr/meta/cur/docs/pdf/2001.4_awanwaves.pdf`
- **SBTSPICE 使用手冊**
PDF格式檔：`/usr/sbt/man/manu.pdf`
PS格式檔：`/usr/sbt/man/manu.ps`
- **SBTPLOT 使用手冊**
PDF格式檔：`/usr/sbt/man/plot.pdf`
PS格式檔：`/usr/sbt/man/plot.ps`
- **問題諮詢**
<http://www.cic.org.tw>



Contents

- 1. SPICE Overview**
- 2. Simulation Input and Controls**
- 3. Sources and Stimuli**
- 4. Analysis Types**
- 5. Simulation Output and Controls**
- 6. Elements and Device Models**
- 7. Optimization**
- 8. Control Options & Convergence**
- 9. Graphic Tools**
- 10. Applications Demonstration**



Class Schedule

⊕ Day1

- SPICE Overview
- Graphic Tools
- Lab1 awaves
- Simulation Input and Controls
- Element Syntax
- Lab2 LPF & Schmitt trigger..
- Sources and Stimuli
- Lab3 Diode_sin & MOS_pwl..
- DC Types Analysis

⊕ Day2

- TRAN & AC Types Analysis
- Lab 4 Differential Amplifier
- Simulation Output and Controls
- Lab 5 High Q Bandpass Filters ...
- Elements and Device Models
- Optimization & Statistical Analysis
- Control Options & Convergence
- Lab 6 RLC circuit test
- Applications Demonstration



Chapter 1

SPICE Overview



Product Development Process

Ideal
想法





Design
設計

Fabrication
製作

Testing
測試

Product
產品

ROM DSP
A/D I/O

    




Circuit Design Background

Circuit/System Design :

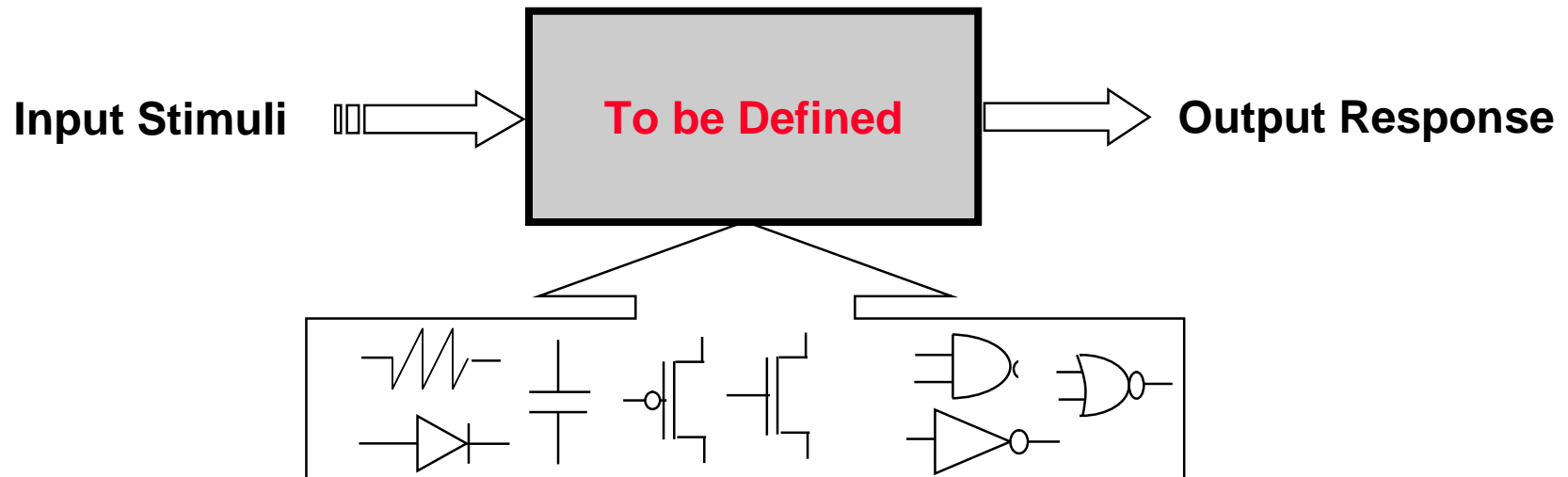
A procedure to construct a **physical structure** which is based on a set of **basic component**, and the constructed structure will provide a **desired function** at specified **time/ time interval** under a given working condition.





What is Simulation

 Simulation : To predict the Circuit/System Characteristic after manufacturing



Depends on the component behavior, simulation categories include :

- Functional simulation
- Logic/Gate Level Simulation
- Switch/Transistor Level Simulation
- **Circuit Simulation**
- Device Simulation

Complexity




Capacity





Circuit Simulation Background

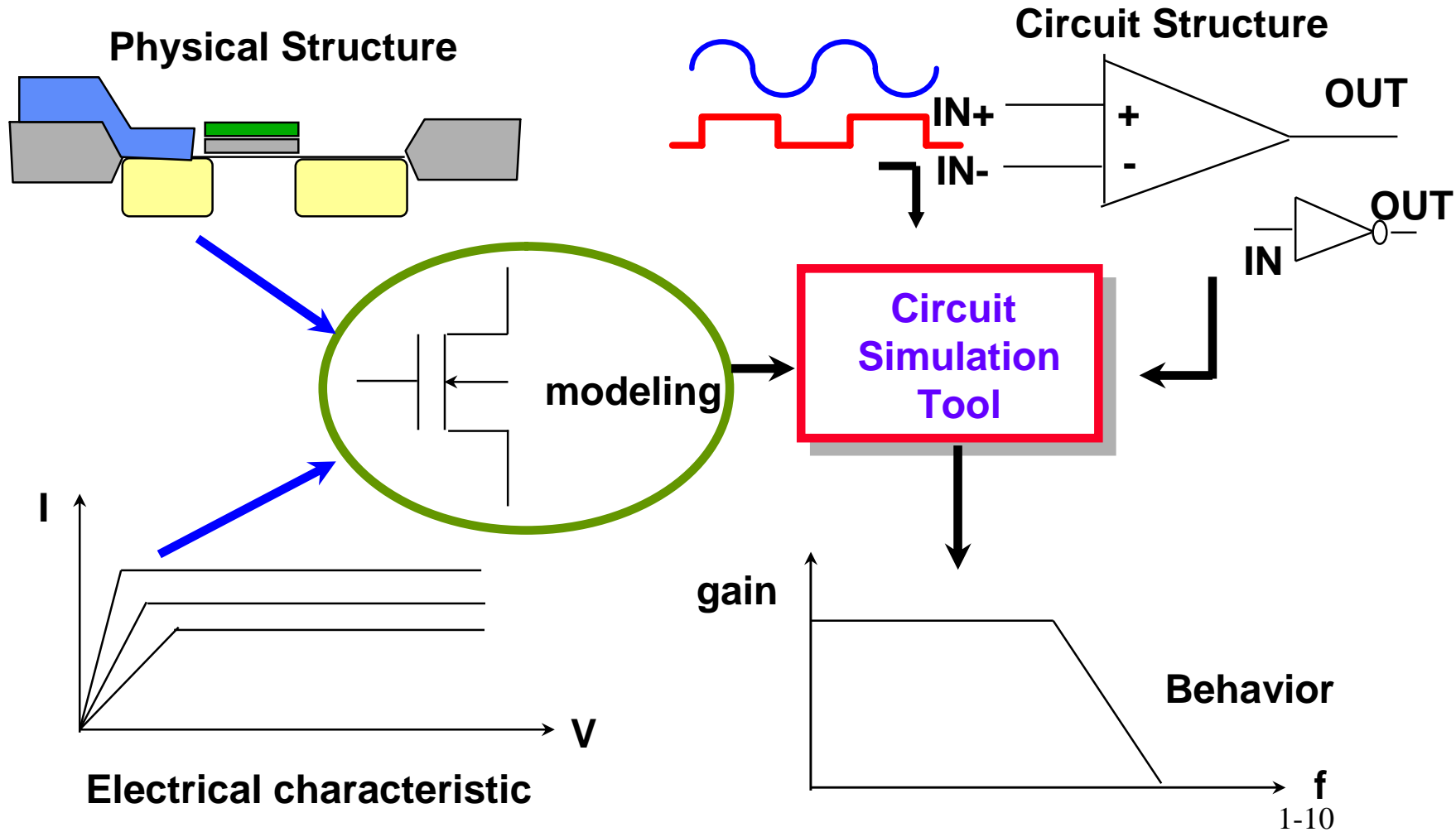



SPICE Background

- **SPICE : Simulation Program with Integrated Circuit Emphasis**
 - Developed by University of California/Berkeley (UCB)
 - Successor to Earlier Effort **CANCER**
 - Widely Adopted, Become **De Facto Standard**
- **Numerical Approach to Circuit Simulation**
 - Circuit Node/Connections Define a **Matrix**
- **Must Rely on Sub-Models for Behavior of Various Circuit Elements**
 - Simple (e.g. **Resistor**)
 - Complex (e.g. **MOSFET**)

Source : IEEE 1997 CICC Educational Sessions, E3.3




SPICE Introduction

- **SPICE generally is a Circuit Analysis tool for Simulation of Electrical Circuits in **Steady-State, Transient, and Frequency Domains.****
- **There are lots of SPICE tools available over the market, **SBTSPICE, HSPICE, Spectre, TSPICE, Pspice, Smartspice, ISpice...****
- **Most of the SPICE tools are originated from **Berkeley's SPICE** program, therefore **support common original SPICE syntax****
- **Basic algorithm** scheme of SPICE tools are similar, however the **control of time step, equation solver and convergence control** might be different.



Solution for Linear Network

 

$$\begin{pmatrix} 0.2 & 0 & -0.1 & -0.1 \\ 0 & 0.2 & -0.2 & 0 \\ -0.1 & -0.2 & 0.5 & -0.2 \\ 0 & 0 & -0.2 & 0.2 \end{pmatrix} \begin{pmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} -3 \\ 3 \\ 0 \\ 0 \end{pmatrix}$$

$$\begin{pmatrix} 0.2 & -0.2 & 0 \\ -0.2 & 0.5 & -0.2 \\ 0 & -0.2 & 0.2 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} 3 \\ 0 \\ 0 \end{pmatrix} \quad V_0 \text{ ground}$$

With Gaussian elimination


$$\begin{pmatrix} 0.2 & -0.2 & 0 \\ 0 & 0.3 & -0.2 \\ 0 & 0 & 0.25 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} 3 \\ 3 \\ 3 \end{pmatrix}$$

Results : $V_3 = 12\text{V}$, $V_2 = 18\text{V}$, $V_1=33\text{V}$



Iteration and approximation - How solution is obtained

Newton-Raphson formula

 

$$I_d = 1\text{pA} * [\exp(40 * V_d) - 1]$$

$$5 = V_d / 2 + I_d$$

$$5 = V_d / 2 + 1\text{pA} * [\exp(40 * V_d) - 1]$$

$$F(V_d) = 0 = -5 + \frac{V_d}{2} + 1\text{pA} * [\exp(40 * v_d) - 1]$$


$$V_{d+1} = V_d - F(V_d) / F'(V_d)$$

	V_d	V_{d+1}	Delta V
1	1	0.975001	0.02499
2	0.975001	0.950002	0.02499
3	0.950002	0.925005	0.02499
4	0.925005	0.900015	0.02499
5	0.900015	0.875041	0.02497
6	0.875041	0.850113	0.02493
7	0.850117	0.825309	0.02481
8	0.825309	0.800838	0.02447
9	0.800838	0.777250	0.02359
10	0.777250	0.755885	0.02136
11	0.755885	0.739445	0.01644
12	0.739447	0.730983	0.00846
13	0.730983	0.729186	0.00179
14	0.729186	0.729119	0.00007

Convergence criteria : Delta V($V_{d+1} - V_d$) < 0.001




SPICE Simulation Algorithm - DC

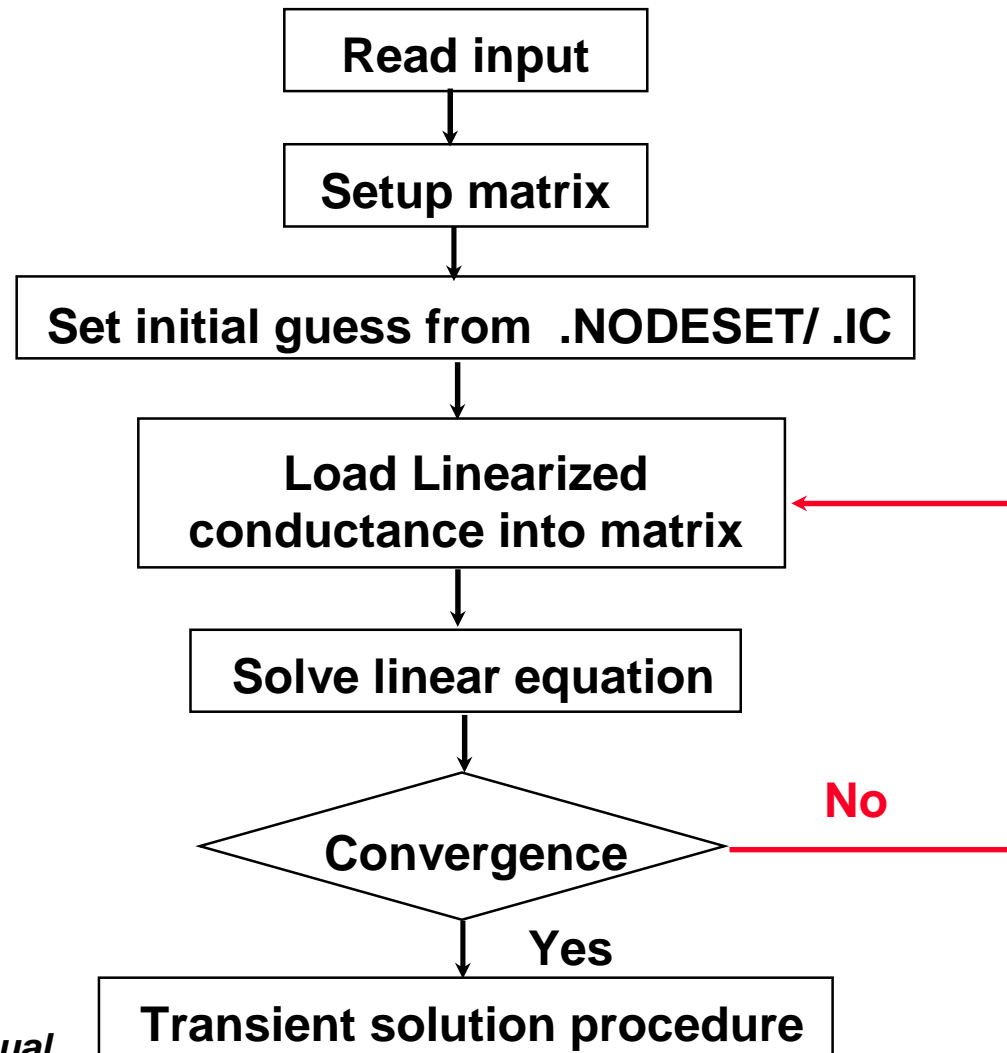



SPICE Simulation Algorithm – Transient

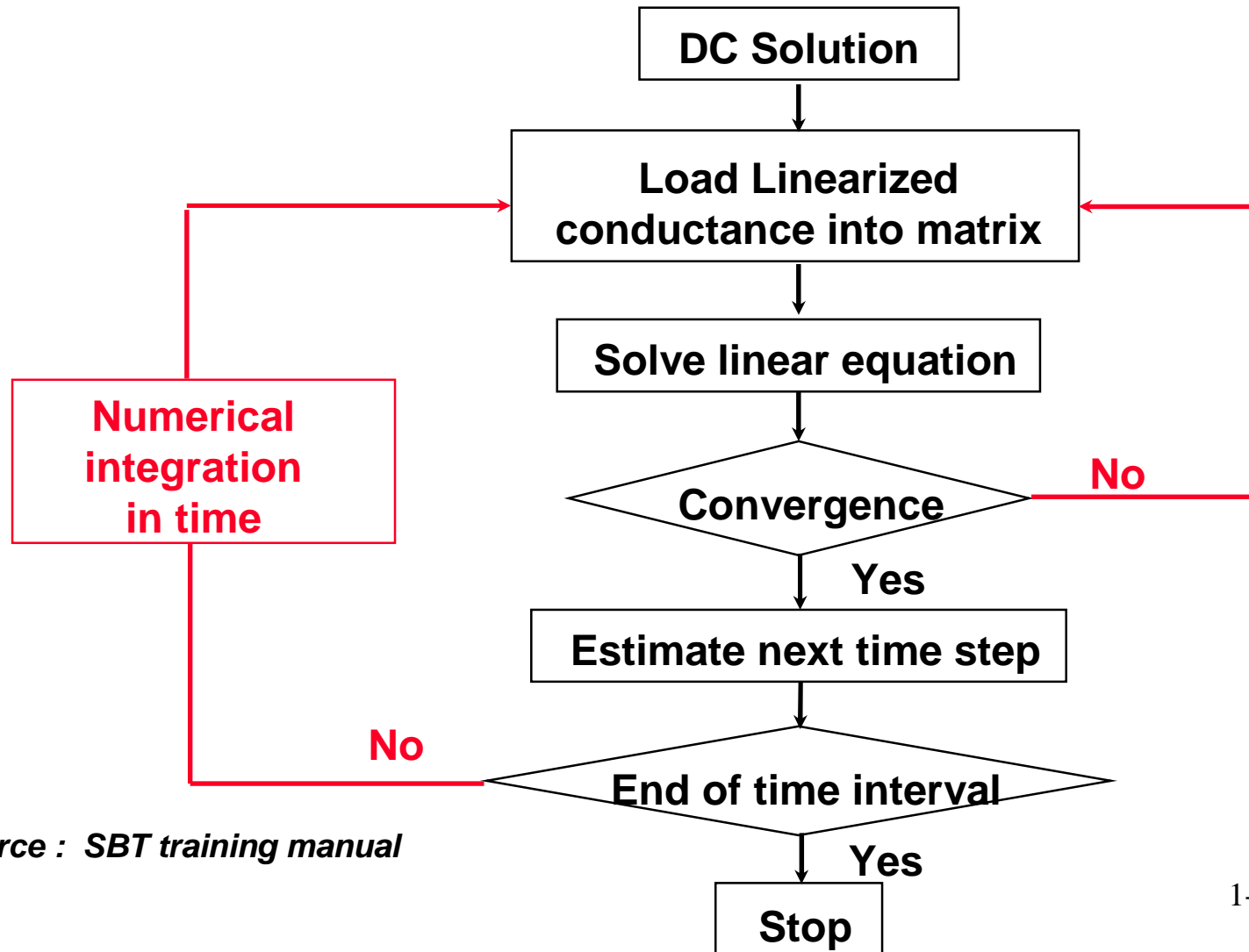

Source : SBT training manual




Basics for Using SPICE Tools

SPICE 之外所需的基本概念

- 了解元件的基本特性
- 熟悉所設計電路的功能
- 了解需要驗證的電路規格及對應的模擬種類及電路組態
- 了解電路的輸入信號特性
- 了解電路各項規格的相依性及優先程度
- 了解電路元件參數與架構對各項電路特性的相關性，以利模擬結果的改進




Basic Flow for SPICE

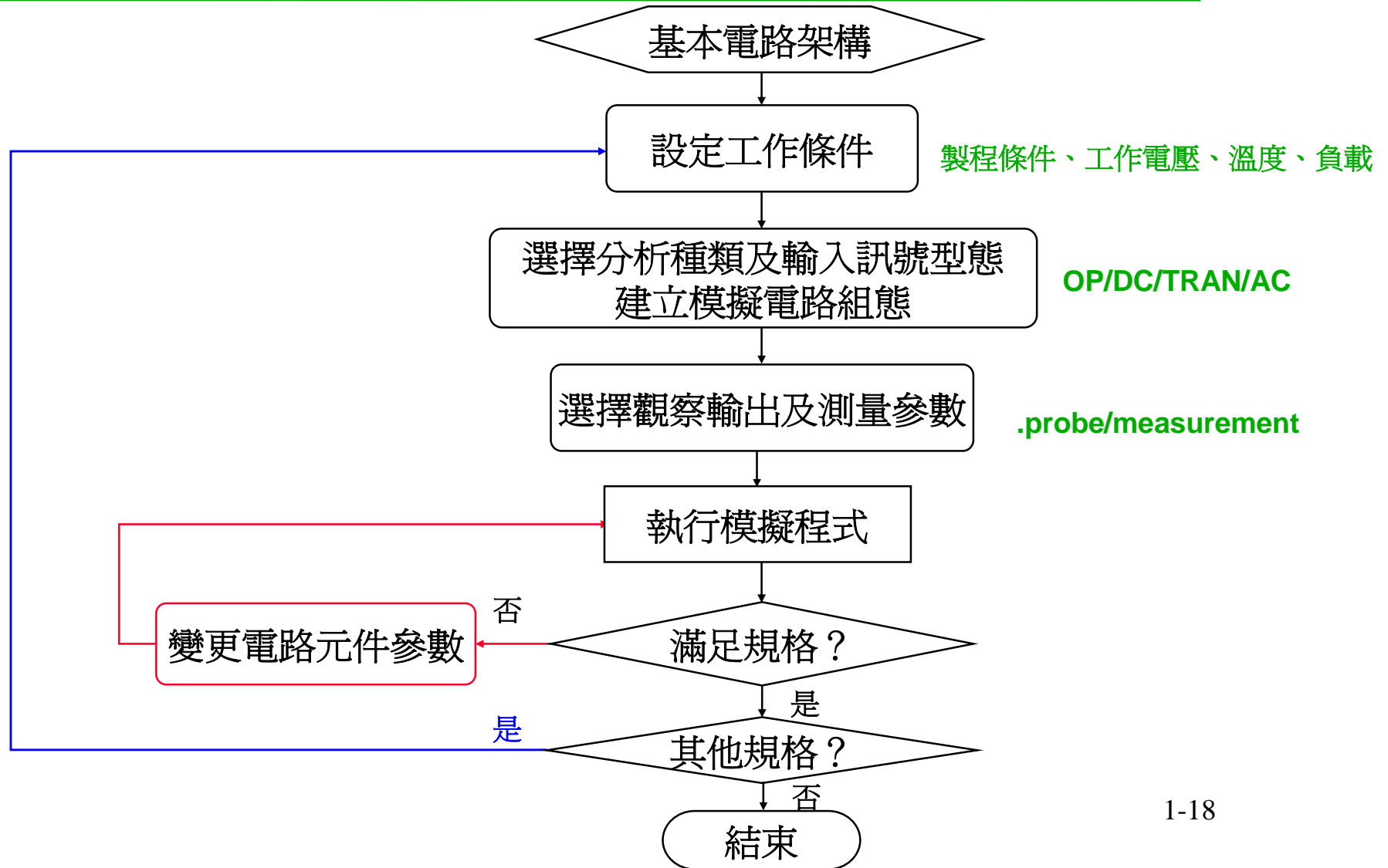



HSPICE GUI

- % hspicegui

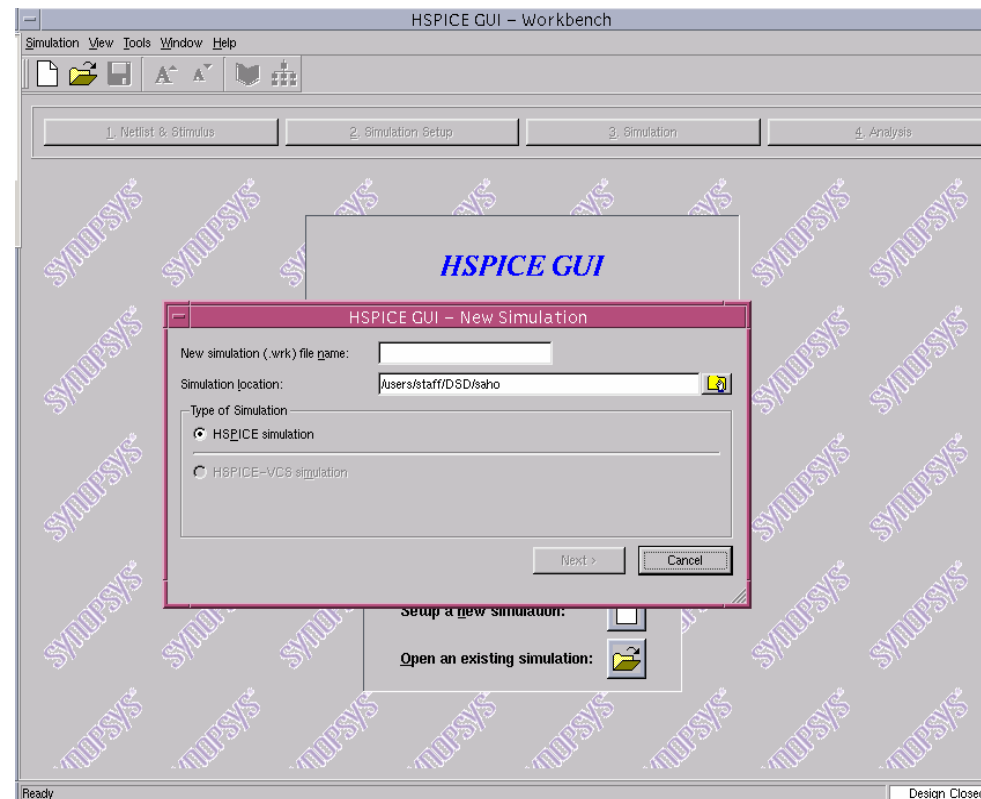



Chapter 2

Graphic Tools



HSPICE 模擬波形觀測介面-awaves簡介

- awaves係視窗程式，需在Xwindow環境下使用。
- 在輸入netlist檔中需指定graphic輸出，hspice才會儲存waveform資料，即加入 `.option post` 的指令項
- 執行awaves 之指令 `/usr/meta/cur/bin/awaves`
- awaves可以顯示 `.sw#` , `.ac#` , `.tr#` , `.mt#` , `.ma#` , `.ms#` , `.ft#` 等模擬結果




Awaves - Awaves Window

menu

Tool button

waveform

 

Data names



Awaves- Open Design

The screenshot shows the 'Open Design' dialog box with the following annotations:

- To path**: Points to the 'History' tab.
- Cd ..**: Points to the left navigation pane.
- File list**: Points to the file list area.
- File list order**: Points to the 'Filter' tab.
- File type to list**: Points to the 'Input' checkbox in the filter menu.
- Set file suffix**: Points to the 'Options...' button in the filter menu.

The dialog box contains a file list with the following items:

- 1.sp
- aa4.2
- aa4.4
- aaaa.sp
- abc.mt0
- abc.sp
- alter2.sp
- Announce

The 'Open:' field is empty. The buttons at the bottom are OK, Apply, Cancel, and Help.



Awaves- Result Browser


The screenshot shows the 'Results Browser' window with the following components and annotations:

- Design:** D0: /users2/cic/wjhsu/HSPICE/tests/m2bit (Annotation: Design name)
- Analysis type in design:** A0 Transient: *file: mos2bit.sp - adder - 2 bit all-nand-gate binary ad
- Hierarchy:** A tree view showing instance names and hierarchy: [IO], x2, x1 (Annotation: Instance name and hierarchy)
- Types:** A list of data types: Time, Voltages (highlighted), TPOWRD, Measures (Annotation: Data type)
- Curves:** A list of data to be shown: v(4), v(12), v(14), v(22), v(24) (Annotation: Data to be shown)
- Current X-Axis:** TIME (Annotation: Set X axis)
- Filter:** *
- Buttons:** Apply, Default, Close, Help



Awaves - Measurement

On window measurement function

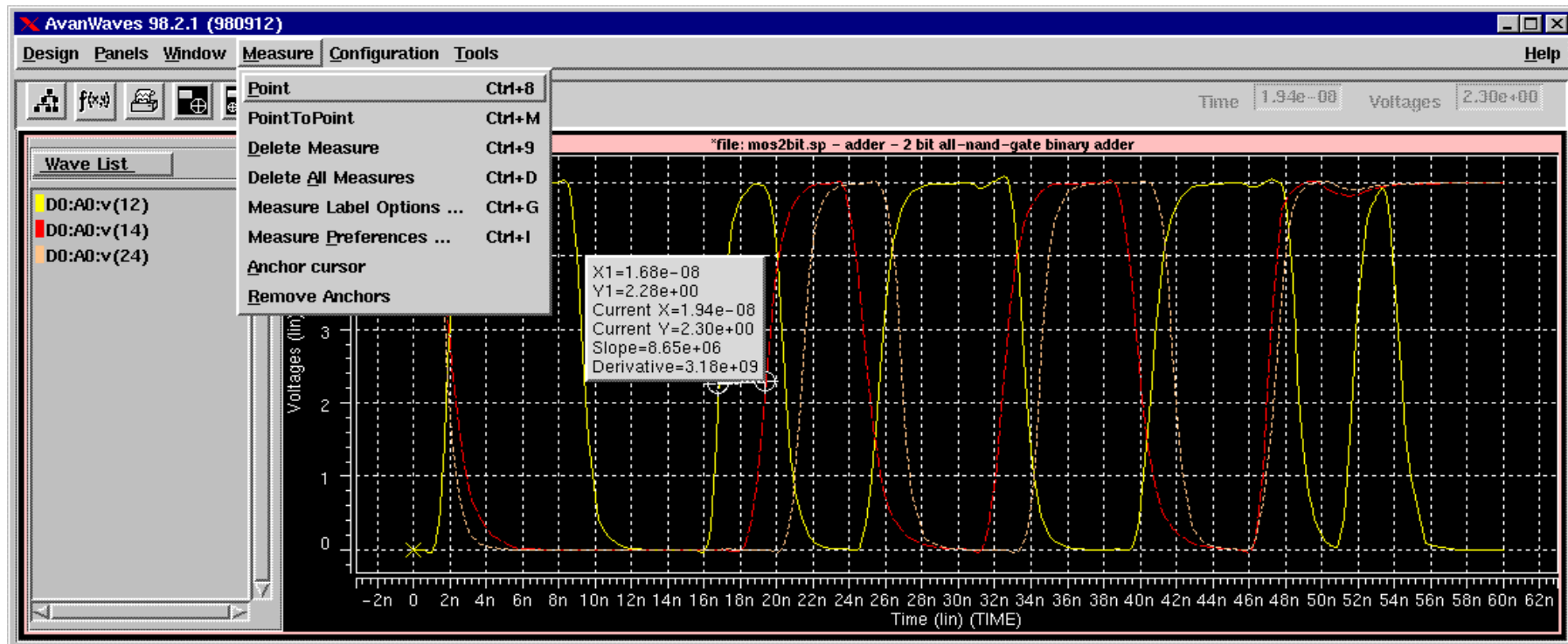




Awaves - Multiple Panels

The screenshot displays the Awaves 98.2.1 (980912) software interface. The main window contains two panels of waveforms. The top panel shows multiple signals (yellow, red, and blue) over time, with a title bar indicating the file path: *file: mos2bit.sp - adder - 2 bit all-nand-gate binary adder. The bottom panel shows a single yellow signal over time, also with the same title bar. A context menu is open over the top panel, listing actions such as Add (Ctrl+A), Hide (Ctrl+1), Delete Panel (Ctrl+Del), Delete Curves (Del), Update (Ctrl+U), Add label... (Ctrl+L), and Delete label (Ctrl+2). The Wave List panel on the left shows the signal DO:A0:v(24). The Time and Voltages scales are visible at the top right of the window.



Awaves - View Port Management


Zoom size is independent between panels

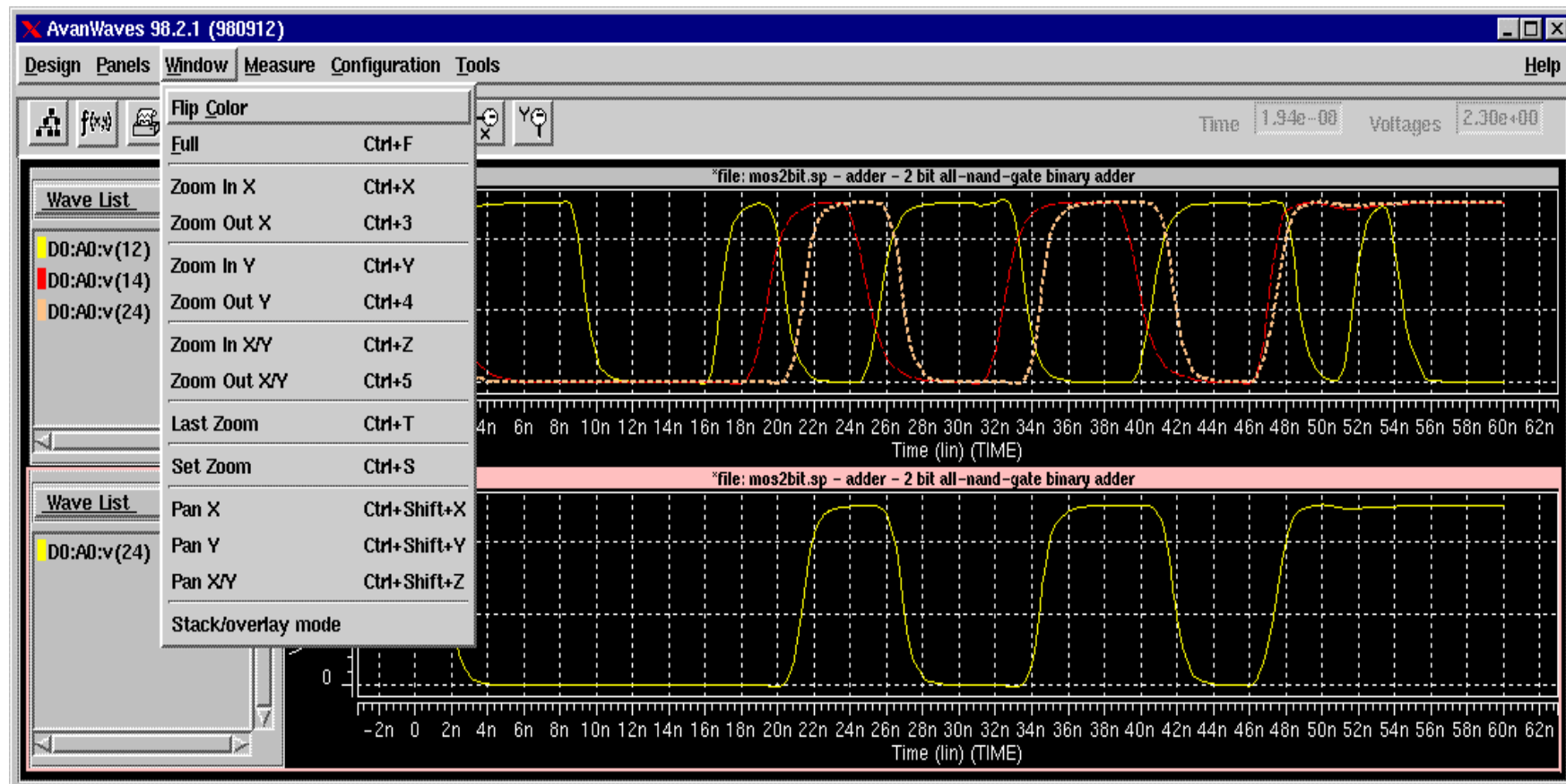



Awaves - Expressions

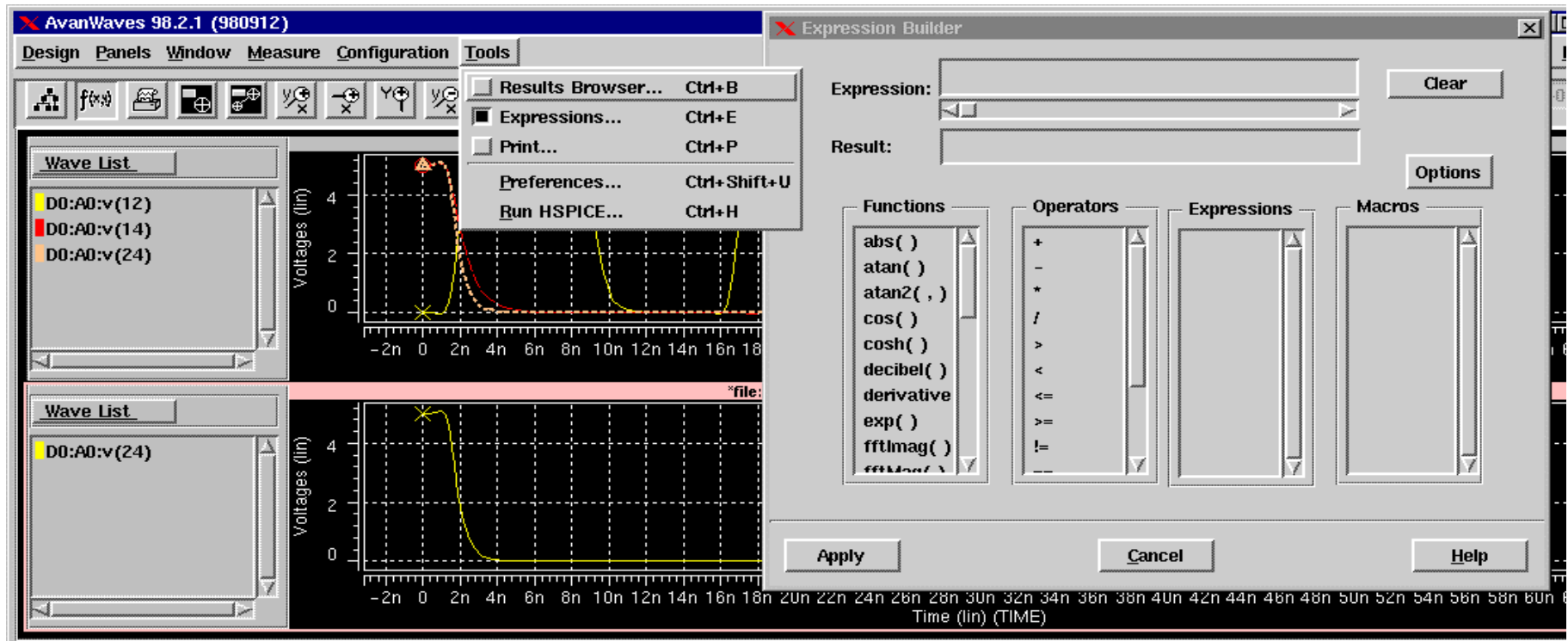Expressions provide capability for data calculation
Can use drag&drop to type expression





Lab1_Awaves

View simulation results with awaves.

Open **inv.readme**


more inv.readme

info: *** hspice job concluded**

HSPICE job inv.sp completed

cic13> ls

inv.ic0 inv.pa0 inv.sp inv.st0 inv.tr0

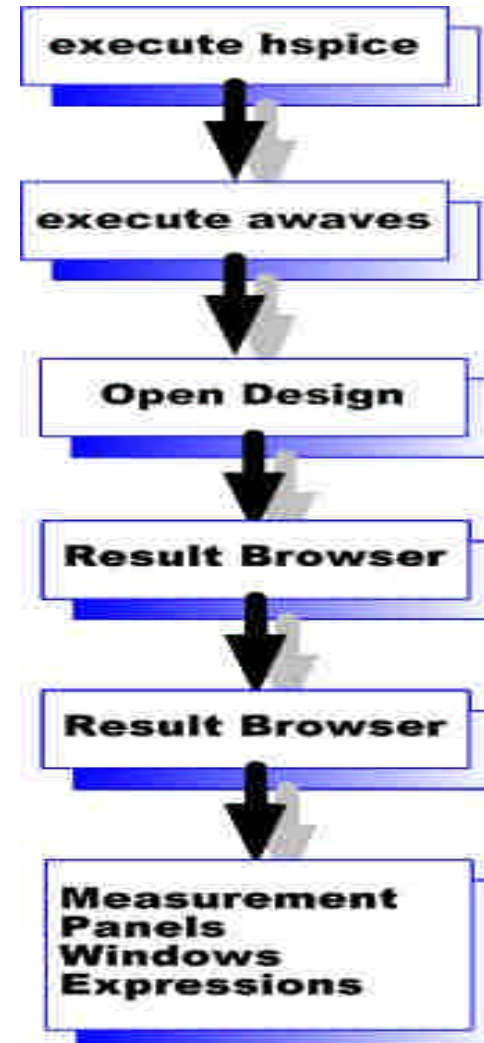




Chapter 3

Simulation Input and Controls



HSPICE Data Flow
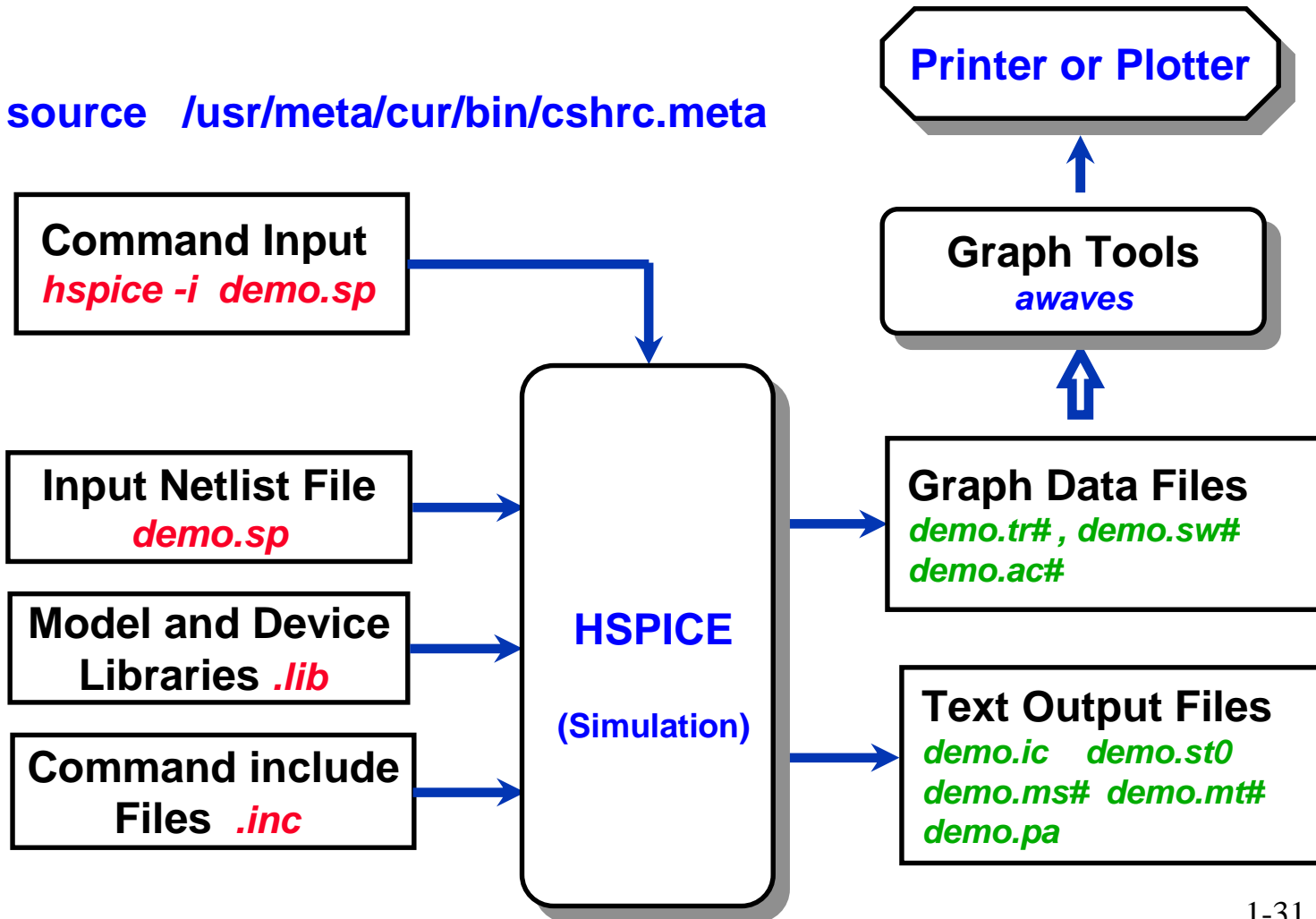
```
source /usr/meta/cur/bin/cshrc.meta
```





Netlist Statements and Elements

TITLE	First line is Input Netlist File Title
* or \$	Commands to Describe Circuit
.OPTIONS	Set Conditions for Simulation
Analysis(AC,DC,TRAN..) & .TEMP	Statements to Set Sweep Variables
.PRINT/.PLOT/.PROBE/.GRAPH	Set Print, Plot, and Graph Variables
.IC or .NODESET	Sets Initial State
.VEC `digital_vector_file`	Sets Input Stimuli File
Sources (I or V)	Sets Input Stimuli
Schematic Netlist	Circuit Description
+	In first Column ,+, is Continuation Char.
.SUBCKT/.ENDS	Sets/Ends Subcircuit Description
.MEASURE (Optimization Optional)	Provides Scope-like Measurement Capability
.LIB or .INCLUDE	Call Library or General Include Files
.MODEL Library	Element Model Descriptions
.DATA or .PARAM	Specify parameters or Parametric Variations
.ALTER	Sequence for In-line Case Analysis
.DELETE LIB	Remove Previous Library Selection
.END	Required Statement to Terminate Simulation



Netlist Structure (SPICE Preferred)

Title -----> **Title Statement - Ignored during simulation**

Components -----> *** Components**

 ┌-----> **c2 2 0 2pf**

 ├-----> **r1 1 0 1k**

 ├-----> **m1 1 2 3 4 mod L=10u W=30u**

 └-----> **x3 2 3 INV**

Models & Subckts -----> ***Model & Subcircuit**

.model... or .LIB or .Subckt

Sources -----> *** voltage sources**

 ┌-----> **v3 3 0 dc 0 ac 0 0 pulse 0 1 0 0.1 0.1 4 8**

 ├-----> **vin in 0 sin(0 2 10k 0.5 0)**

Controls -----> **.option nomod nopage**

 ┌-----> **.tran 1 10**

 ├-----> **.print v(5) i(r1)**

 └-----> **.plot v(3) v(in)**

End file -----> **.end**



Element and Node Naming Conventions

● Node and Element Identification:

- Either Names or Numbers (e.g. data1, n3, 11,)
- **0 (zero)** is Always Ground
- ★ ■ Trailing Alphabetic Character are ignored in Node Number, (e.g. **5A=5B=5**)
- Ground may be 0, GND, !GND
- All nodes are assumed to be local
- Node Names can be may Across all Subcircuits by a **.GLOBAL** Statement (e.g. **.GLOBAL VDD VSS**)



Element and Node Naming Conventions (Cont.)

● Instance and Element Names:

C	Capacitor
D	Diode
E,F,G,H	Dependent Current and Voltage Controlled Sources
I	Current
J	JFET or MESFET
K	Mutual Inductor
L	Inductor
M	MOSFET
Q	BJT
R	Resistor
O,T,U	Transmission Line
V	Voltage Source
X	Subcircuit Call

● Path Names of Subcircuits Nodes: e.g. V(X1.net1), I(X1.X4.net3),I(X2.Mn0)



Units and Scale Factors

- **Units:**

R Ohm (e.g. R1 n1 n2 1K)
C Farad (e.g. C2 n3 n4 1e-12)
L Henry (e.g. L3 n5 n6 1e-9)

- **Scale Factors :**

F	1e-15
P	1e-12
N	1e-9
U	1e-6
M	1e-3

K	1e3
Meg	1e6
G	1e9
T	1e12
DB	20log ₁₀

Examples:
1pF
1nH
10Meg Hz
vdb(v3)

Warning: in SBTSPICE 1.e-15F , will be interpreted as 1e-15 fento Farad

- **Technology Scaling :** All Length and Widths are in **Meters**

Using `.options scale=1e-6` → L=2 W=100



Library Input Statement

- **.INCLUDE Statement** Copy the content of file into netlist

```
.INCLUDE '$installdir/parts/ad'
```

- **.LIB Definition and Call Statement** File reference and Corner selection

```
.LIB TT ← Corner name  
.MODEL nmos_tt nmos (level=49 Vt0=0.7  
+TNOM=27 .....)  
.ENDL TT
```

```
.LIB '~users/model/tsmc/logic06.mod' TT ← Corner name
```

- **.PROTECT** ← **Prevent the listing of included contents**
.LIB "~users/model/tsmc/logic06.mod" *TT*
.UNPROTECT



Hierarchical Circuits, Parameters, and Models

● **.SUBCKT Statement : Description**

■ **.SUBCKT Syntax**

.SUBCKT subname n1 <n2 n3...> <param=val...>

n1 ... Node Number for External Reference; Cannot be **Ground node (0)**

Any Element Nodes Appearing in Subckt but not Included in this list are Strictly **LOCAL**, with these **Exceptions** :

(1) **Ground Node (0)**

(2) Nodes Assigned using **.GLOBAL** Statement

(3) Nodes Assigned using **BULK=node** in MOSFET or BJT Models

param Used **ONLY** in Subcircuit, **Overridden** by Assignment in Subckt Call or by values set in **.PARAM** Statement

.ENDS [subname]



Hierarchical Circuits, Parameters, and Models (Cont.)

● .SUBCKT Statement : Examples

```
* subckt exampels
.PARAM VALUE=5V WN=2u WP=8u
*set up invert's sub-circuit
.SUBCKT INV IN OUT WN=2u WP=8u
M1 OUT IN VDD VDD PCH L=0.5u W=WP
M2 OUT IN 0 0 NCH L=0.5u W=WN
R1 OUT 4 1K
R2 4 5 10K
.ENDS INV
* call sub-circuit INV
X1 1 2 INV WN=5u WP=20u
*.LIB Definition and Call Statement
.lib 'mm0355v.l' tt
* input signal
vin in 0 pulse (0 3.3 0 1n 1n 49n 100n)
*.tran type analysis
.tran 50n 1u
.end
```



Hierarchical Circuits, Parameters, and Models (Cont.)

■ Subcircuit Calls (X Element Syntax)

Xyyyy n1 <n2 n3...> subname <param=val...> <M=val>

XNOR3 *ina inb inc out NOR WN=3u LN=0.5u M=2*

```
subckt - 記事本
檔案(F) 編輯(E) 格式(O) 說明(H)
1 ***** HSPICE -- U-2003.09 (20030718) 13:33:24 03/05/2004 pc
*****
* subckt exampels
***** circuit name directory
*****
circuit number to circuit name directory
number circuitname          definition      multiplier
  0 main circuit
  1 x1.                      inv           1.00

1 ***** HSPICE -- U-2003.09 (20030718) 13:33:24 03/05/2004 pc
*****
```




Input Control Statements: **.TEMP**

● **.TEMP Statement: Description**

- When TNOM is not Specified, it will Default to **25 °C** for HSPICE
When TNOM is not Specified, it will Default to **27 °C** for SBTSPICE

■ Example 1:

```
.TEMP 30 $ Ckt simulated at 30 °C
```

■ Example 2:

```
.OPTION TEMP = 30 $ Ckt simulated at 30 °C
```

■ Example 3:

```
.TEMP 100
```

```
D1 n1 n2 DMOD DTEMP=30 $ D1 simulated at 130 °C
```

```
D2 n3 n4 DMOD $ D2 simulated at 100 °C
```

```
R1 n5 n6 1K
```

HSPICE : DTEMP
SBTSPICE : TEMP



Input Control Statements : **.ALTER**

- **.ALTER Statement : Description**

- **Rerun a Simulation Several Times with Different**

**Circuit Topology
Models
Elements Statement
Parameter Values
Options
Analysis Variables, etc.**

- **1st Run : Reads Input Netlist File up to the first .ALTER**
- **Subsequent : Input Netlists to next .ALTER, etc.**



Input Control Statements : **.ALTER (Cont.)**

● **.ALTER Statement : Example**

```
*file2: alter2.sp  alter examples  $ Title Statement
.lib 'mos.lib' normal
.param wval=50u Vdd=5V
r4 4 3 100
:
.alter
.del lib 'mos.lib' normal          $ remove normal model lib
. lib 'mos.lib' fast              $ get fast model lib
.alter
.temp -50 0 50                   $ run with different temperature
r4 4 3 1K                         $ change resistor value
c3 3 0 10p                       $ add the new element
.param wval=100u Vdd=5.5V        $ change parameters
.end
```



Input Control Statements : .ALTER (Cont.)

● .ALTER Statement : Limitations

■ CAN Include:

- ➔ Element Statement (Include Source Elements)
- ➔ .DATA, .LIB, .INCLUDE, .MODEL Statements
- ➔ .IC, .NODESET Statement
- ➔ .OP, .PARAM, .TEMP, .TF, .TRAN, .AC, .DC Statements

■ CANNOT Include:

- ➔ .PRINT, .PLOT, .GRAPH, or any I/O Statements



Input Control Statements: .DATA

- **.DATA Statement:**

Operating point: `.DC DATA=dataname`

DC sweep: `.DC vin 1 5 .25 SWEEP DATA=dataname`

AC sweep: `.AC dec 10 100 10meg SWEEP DATA=dataname`

TRAN sweep: `.TRAN 1n 10n SWEEP DATA=dataname`

```
.DATA dataname pnam1 <pnam2 pnam3 ... pnamxxx >  
+ pval1<pval2 pval3 ... pvalxxx>  
+ pval1' <pval2' pval3' ... pvalxxx'>  
.ENDDATA
```



Input Control Statements: .DATA (cont.)

● .DATA Statement: Inline or Multiline .DATA Example

Inline .DATA Example

```
.TRAN 1n 100n SWEEP DATA=devinf
.AC DEC 10 Hz 100khz SWEEP DATA=devinf
.DC TEMP -55 125 10 SWEEP DATA=devinf
*
.DATA devinf Width Length Vth Cap
+          10u   100u   2v   5p
+          50u   600u  10v  10p
+          100u  200u   5v  20p
.....
.ENDDATA
```

Multiline .DATA Example

```
.PARAM Vds=0 Vbs=0 L=1.0u
.DC DATA=vdot
.DATA vdot
Vbs Vds L
0 0.1 1.0u
0 0.1 1.5u
-1 0.1 1.0u
0 0.5 1.0u
.....
.ENDDATA
```



Input Control Statements: **.OPTION**

● **.OPTION Statement : Description**

■ **.Option Controls for**

Listing Formats
Simulation Convergence
Simulation Speed
Model Resolution
Algorithm
Accuracy

■ **.Option Syntax and Example**

```
.OPTION opt1 <opt2> .... <opt=x>
```

```
.OPTION LVLTIM=2 POST PROBE SCALE=1
```



Input Control Statements: **.OPTION(Cont.)**

● **.OPTION Keywords Summary :**

■ **General Control Options**

*Input, Output
CPU
Interfaces
Analysis
Error
Version*

■ **Model Analysis**

*General
MOSFETs
Inductors
BJTs
Diodes*

■ **DC Operating Point and DC Sweep Analysis**

*Accuracy
Matrix
Input, Output
Convergence
Pole/Zero*

■ **Transient and AC Small Signal Analysis**

*Accuracy
Speed
Timestep
Algorithm
Input, Output*




Lab2_ low-pass filter

Exercise 1 low-pass filter



View simulation results with awaves and lpf.lis file

Follow lpf.readme

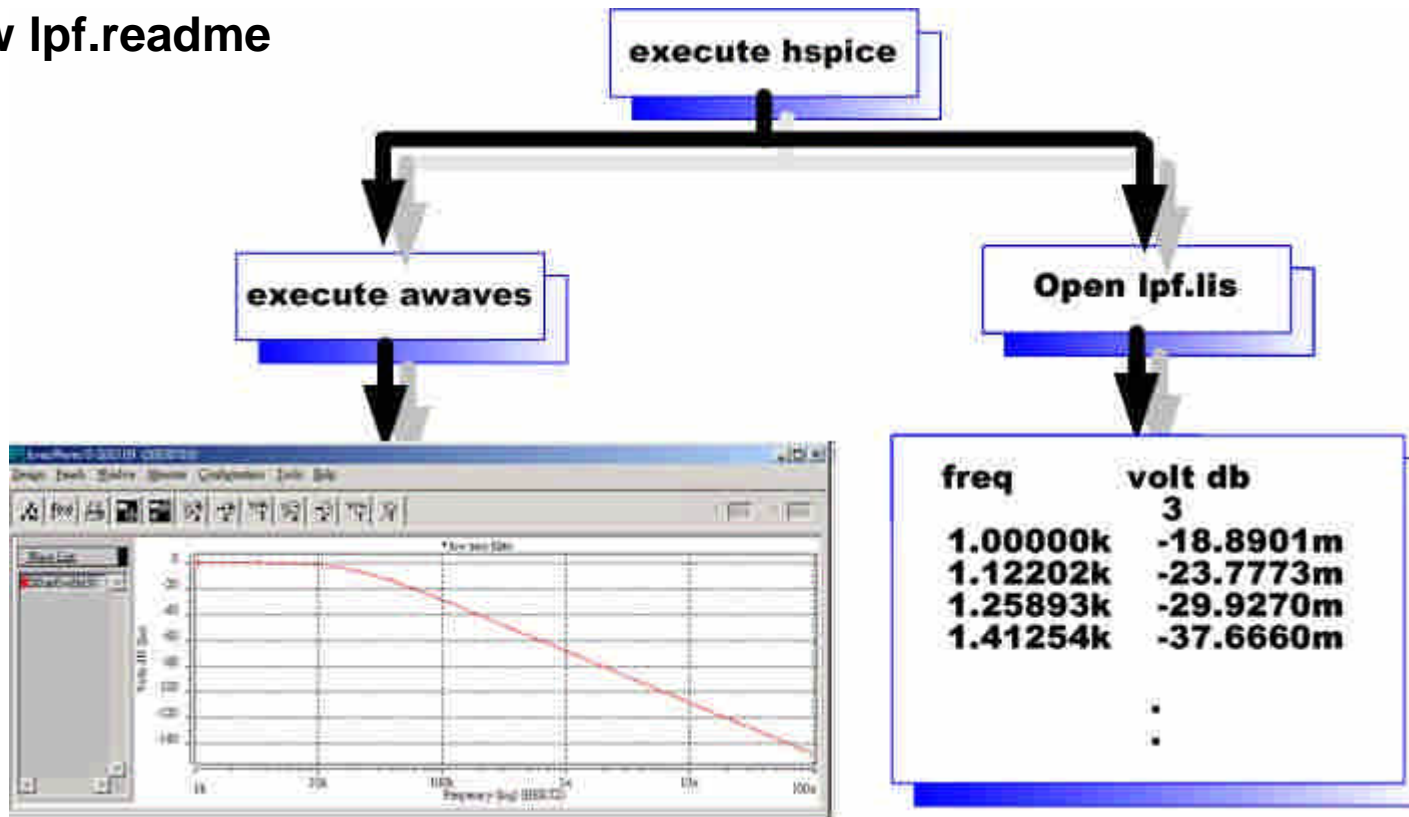




Lab2_ Schmitt trigger

Exercise2 Schmitt trigger

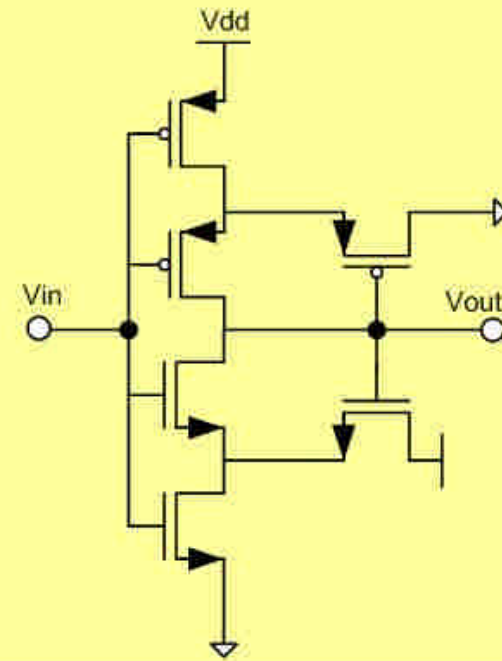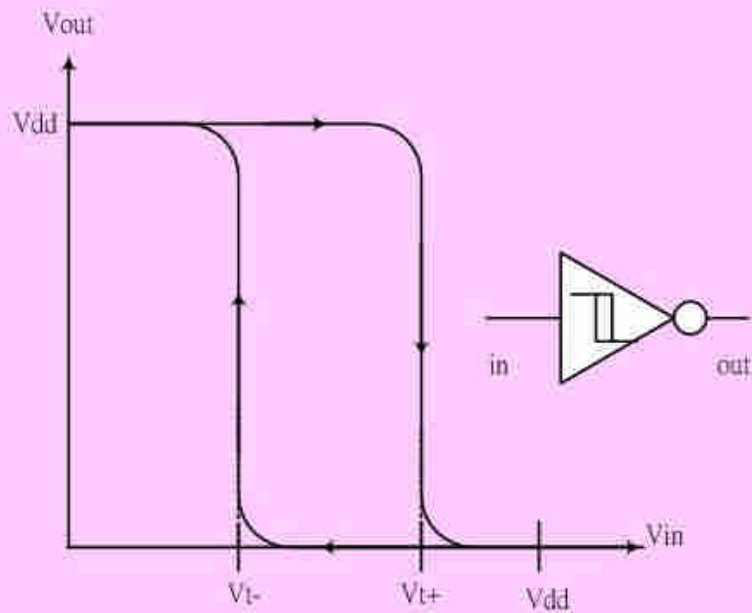



Lab2_ Schmitt trigger

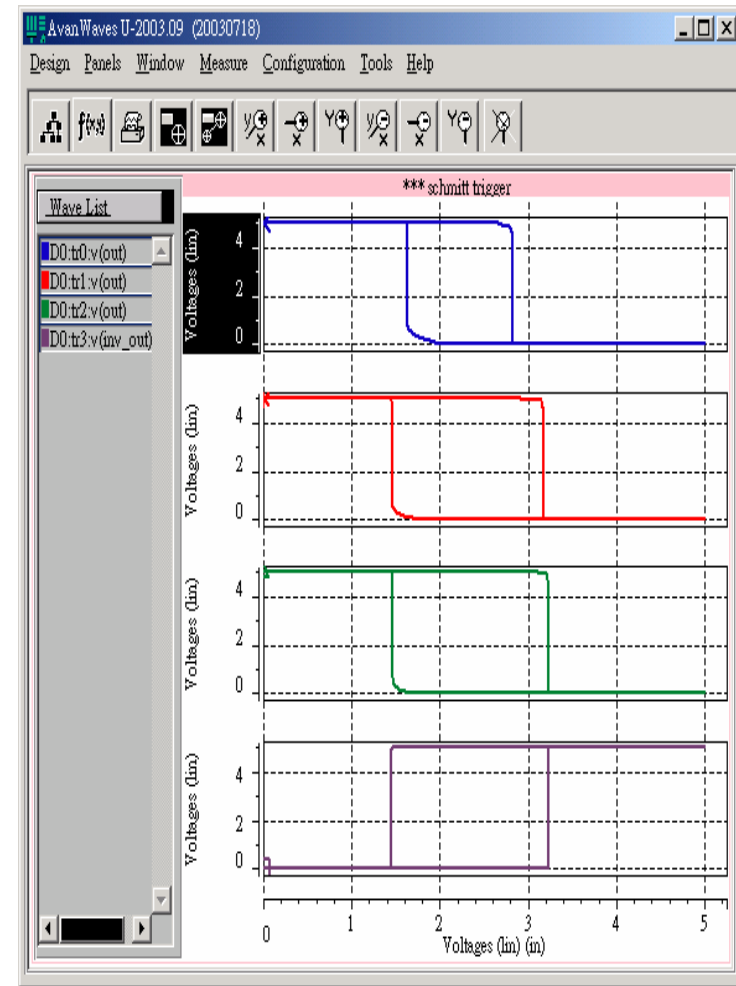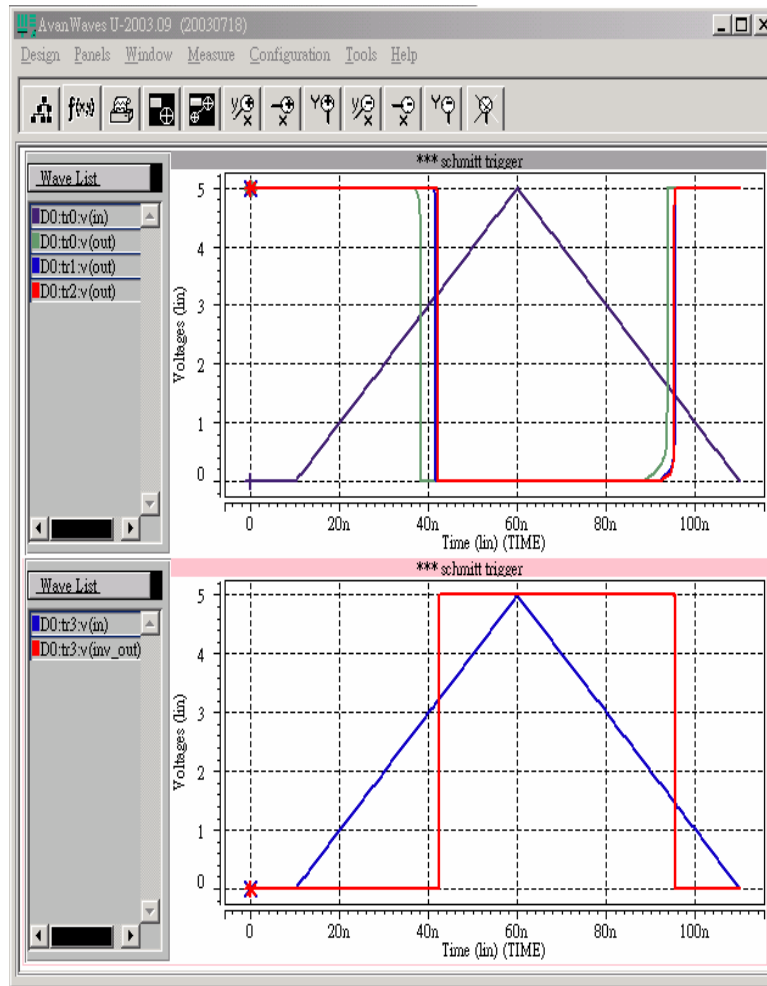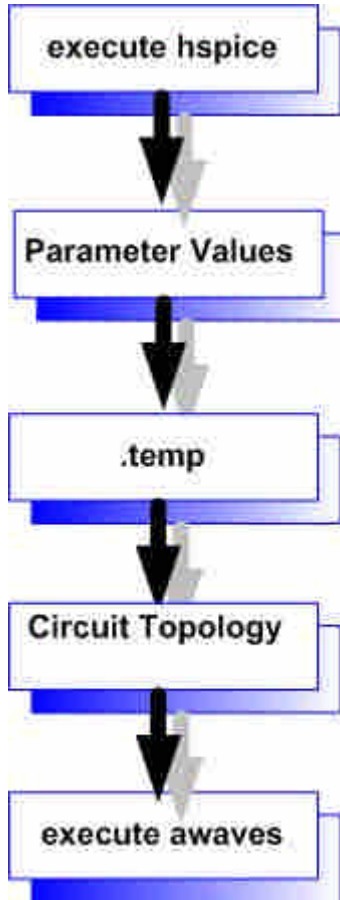

Follow [Schmitt_trigger.readme](#)



Chapter 4

Sources and Stimuli



Source / Stimuli : 提供電路驅動來源

1. 固定值獨立電源

提供固定偏壓或固定驅動電流

2. 時變/頻變 獨立電源

提供變動的電壓或電流輸入，一般供輸入信號用

3. 時變/頻變 壓控/源控 相依電源

提供可控制的電壓或電流源，一般供建立模型用

壓控電壓源(VCVS) -- *E Elements*

壓控電流源(VCCS) -- *G Elements*

流控電壓源(CCVS) -- *H Elements*

流控電流源(CCCS) -- *F Elements*



AC, DC Sources

- **Source Element Statement :**

- **Syntax :**

```
Vxxx n+ n- < <DC=>dcval> <tranfun> <AC=acmag, <acphase>>  
lyyy n+ n- < <DC=>dcval> <tranfun> <AC=acmag, <acphase> <M=val>
```

- **Examples of DC & AC Sources :**

```
V1 1 0 DC=5V  
V2 2 0 5V  
I3 3 0 5mA
```

```
V4 4 0 AC=10V, 90  
V5 5 0 AC 1.0 180
```

***AC or Freq. Response Provide Impulse Response**

- **Examples of Mixed Sources :**

```
V6 6 0 5V AC=1V, 90  
V7 7 0 0.5V AC 1.0 SIN (0 1 1Meg)
```



Transient Sources

- **Types of Independent Source Functions :**

Pulse (**PULSE** Function)

Sinusoidal (**SIN** Function)

Piecewise Linear (**PWL** Function)

Exponential (**EXP** Function)

Single-Frequency FM (**SFFM** Function)

Single-Frequency AM (**AM** Function)




Pulse Source Function

■ Syntax :

PULSE (*V1* *V2* < *Tdelay* *Trise* *Tfall* *Pwidth* *Period* >)

■ Example :

 ***Vin* 1 0 *PULSE* (0V 5V 10ns 10ns 10ns 40ns 100ns)**





Sinusoidal Source Function


■ Syntax :

SIN (Voffset Vacmag < Freq Tdelay Dfactor >)

$$\text{Voffset} + \text{Vacmag} * e^{-(t-TD) * Dfactor} * \sin(2\pi \text{Freq}(t-TD))$$

■ Example :

Vin 3 0 SIN (0V 1V 100Meg 2ns 5e7)

 



Piecewise Linear Source Function

■ Syntax :


PWL (<t1 v1 t2 v2> <R<=repeat>> <Tdelay=delay>)

\$ R=repeat_from_what_time TD=time_delay_before_PWL_start

■ Example :

V1 1 0 **PWL** 60n 0v, 120n 0v, 130n 5v, 170n 5v, 180n 0v, R 0

 V2 2 0 **PL** 0v 60n, 0v 120n, 5v 130n, 5v 170n, 0v 180n, R 60n






Specifying a Digital Vector File

■ Syntax :

.VEC 'digital_vector_file'

 

In spice Netlist

The digital vector file consists of three parts:

- **Vector Pattern Definition**
- **Waveform Characteristics**
- **Tabular Data**

■ Digital Vector File Example (ref. adder2.sp):

```
; Vector Pattern  
RADIX 2 2 1  
VNAME A[[1:0]] B[[1:0]] C[0]  
io i i i  
tunit ns
```



Specifying a Digital Vector File(Cont.)

■ Digital Vector File Example (Cont.) :

; **Waveform Characteristics**

slope 1

vil 0

vih 5


tunit ns

; **Tabular Data**

period 10

0 0 0	<i>;</i> t=0	00	00	0
0 1 1	<i>;</i> t=1	00	01	1
0 2 0	<i>;</i> t=2	00	10	0
0 3 1	<i>;</i> t=3	00	11	1
1 0 0		01	00	0
1 1 1		01	01	1
1 2 0		01	10	0
1 3 1	
2 0 0				
2 1 1				

≡ 1
≡ 0

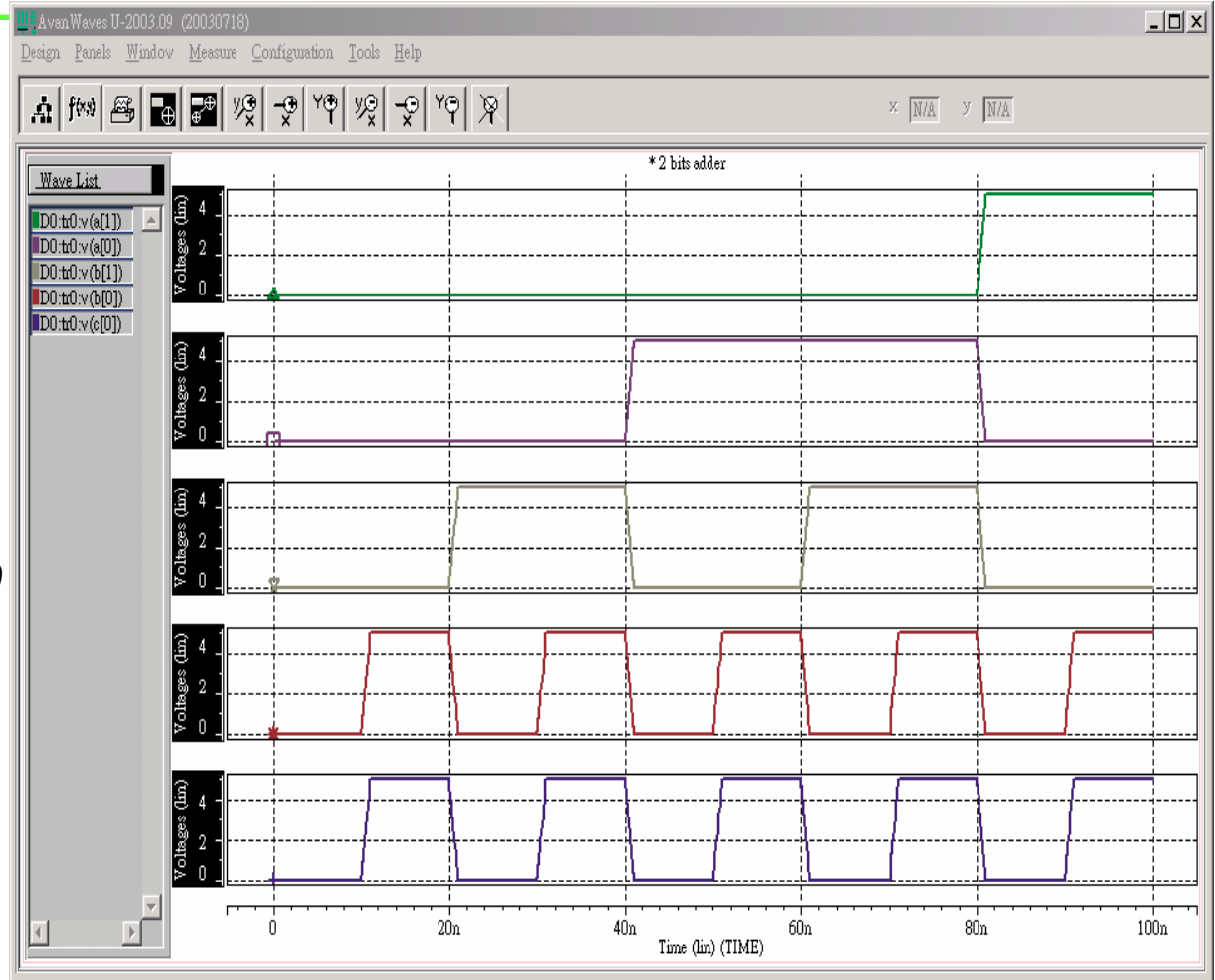



VCVS --- E Elements

■ Syntax :

Linear form

Exxx n+ n- in+ in- gain <MAX=val> <MIN=val> <IC=val>....

■ Example :

*** ideal op-amp example

vin in 0 sin(0 50m 1meg)


EOPA out 0 in 0 max=+5 min=-5 1e3

.tran 10n 1u

.end

Ebuf 2 0 1 0 1.0

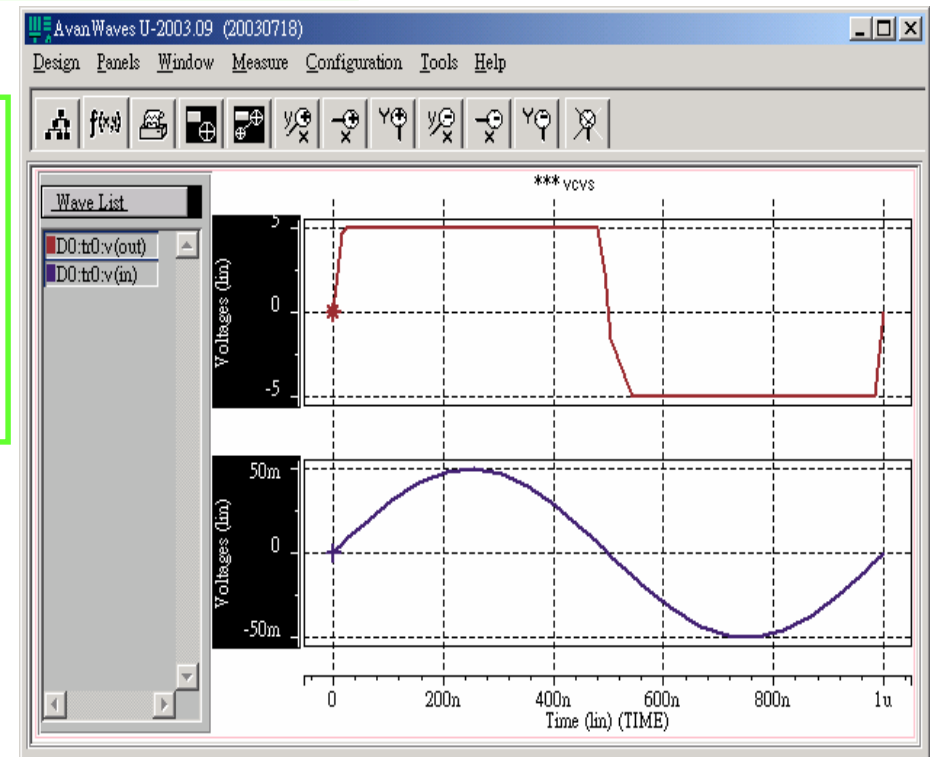- **Polynomial Controlled Sources**
POLY(1), POLY(2), POLY(3)





VCCS --- G Elements

■ Syntax :

Voltage Controlled Resistor (VCR)

Gxxx n+ n- **VCR NPWL(1)** in+ in- <TC1=val>x1,y1 x2,y2 ... <IC=val>

*** NPWLModels the symmetrical bidirectional switch or transfer
*** gate, NMOS

■ Example :

*** Switch-Level MOSFET ***

Gnmos d s **VCR** NPWL(1) g s LEVEL=1 0.4v,150g 1v,10meg 2v,50k
+ 3v,4k 5v,2k


*** Switch ***

Gswitch 2 0 **VCR PWL(1)** 1 0 0v,10meg 1v,1m

■ Voltage Controlled Capacitor (VCCAP)



ICIS --- F Elements




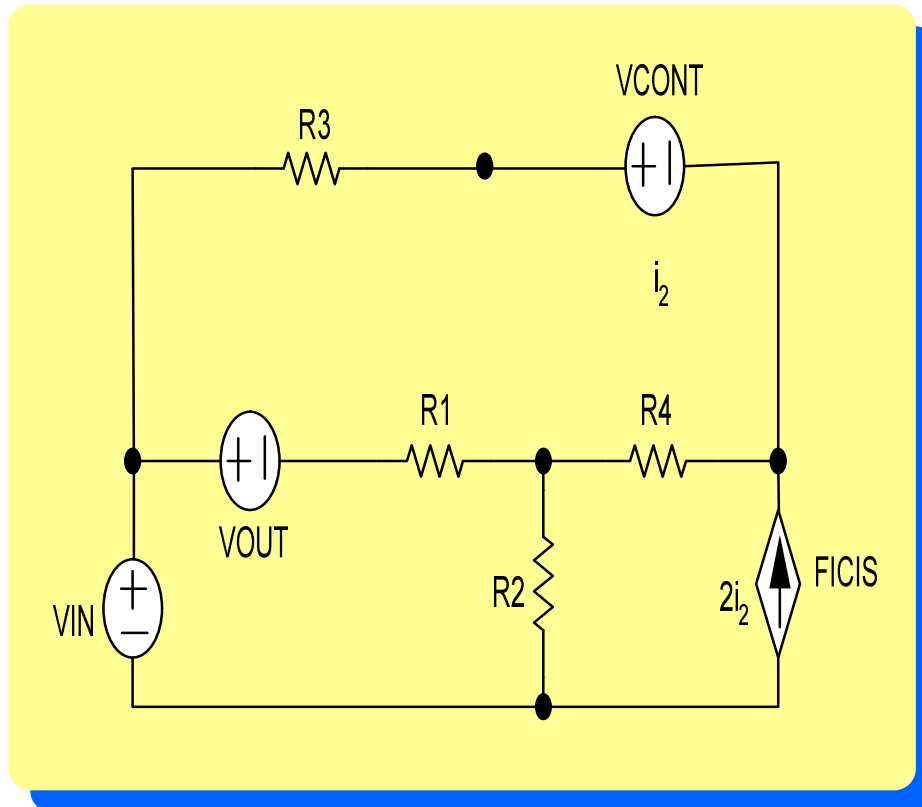


*** icis example

```
vin 1 0 dc 3
r1 5 2 1
r2 2 0 2
r3 1 4 3
r4 2 3 4
vcont 4 3 0
ficis 0 3 vcont 2
vout 1 5 0
.op
.end
```



Switch Capacitor Amplifier

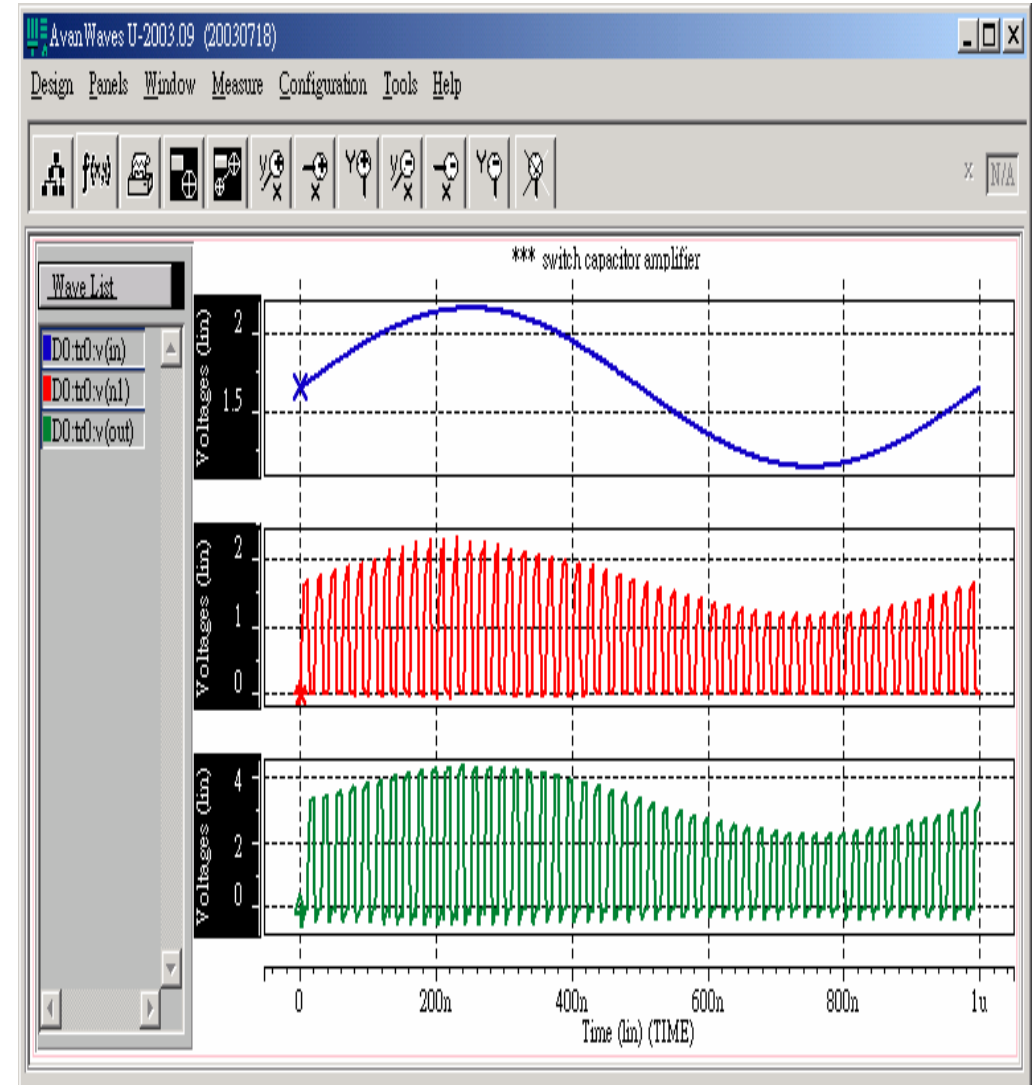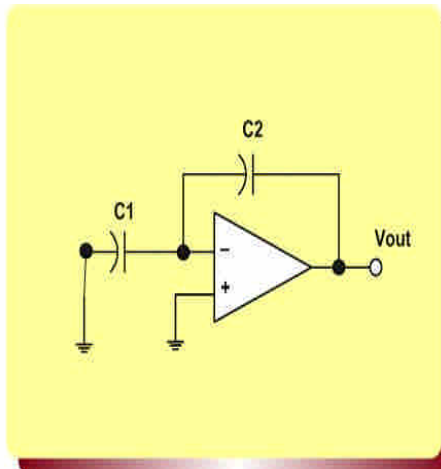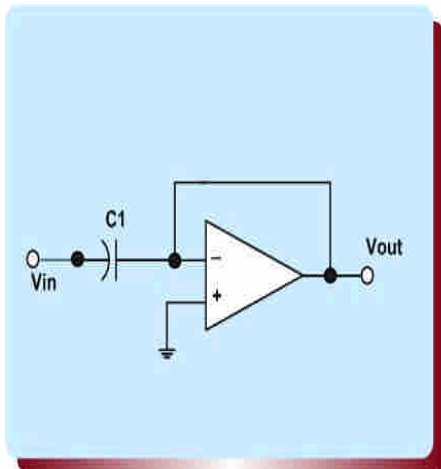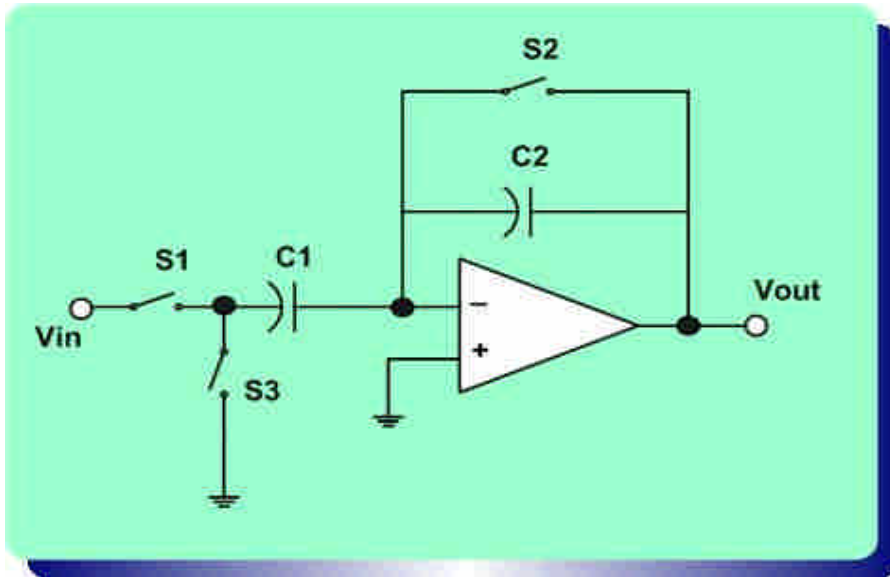



Switch Capacitor Amplifier


```
*** switch capacitor amplifier
eopamp out 0 inb ina 1e4 * opa element
c1 n1 ina 2p
c2 ina out 1p
gsw1 in n1 VCR NPWL(1) phi1 in LEVEL=1 0.1,1e+28 .2,4k 1,2.8k 3,841 5,495
gsw2 ina out VCR NPWL(1) phi1 ina LEVEL=1 0.1,1e+28 .2,4k 1,2.8k 3,841 5,495
gsw3 n1 0 VCR NPWL(1) phi2 n1 LEVEL=1 0.1,1e+28 .2,4k 1,2.8k 3,841 5,495
*** gsw1, gsw2,gsw3 Switch-Level MOSFET
*** voltage sources, clock signals
vin in 0 sin(1.65 0.5 1meg)
vinb inb 0 0
vphi1 phi1 0 pulse(0 5 1n 1n 1n 9n 20n)
vphi2 phi2 0 pulse(5 0 1n 1n 1n 9n 20n)
*** transient type simulation
.tran 10n 1u
*** set environment
.option post
.end
```




Lab3 Diode_sin & MOS_pwl

View simulation results with awaves.

diode_sin.sp

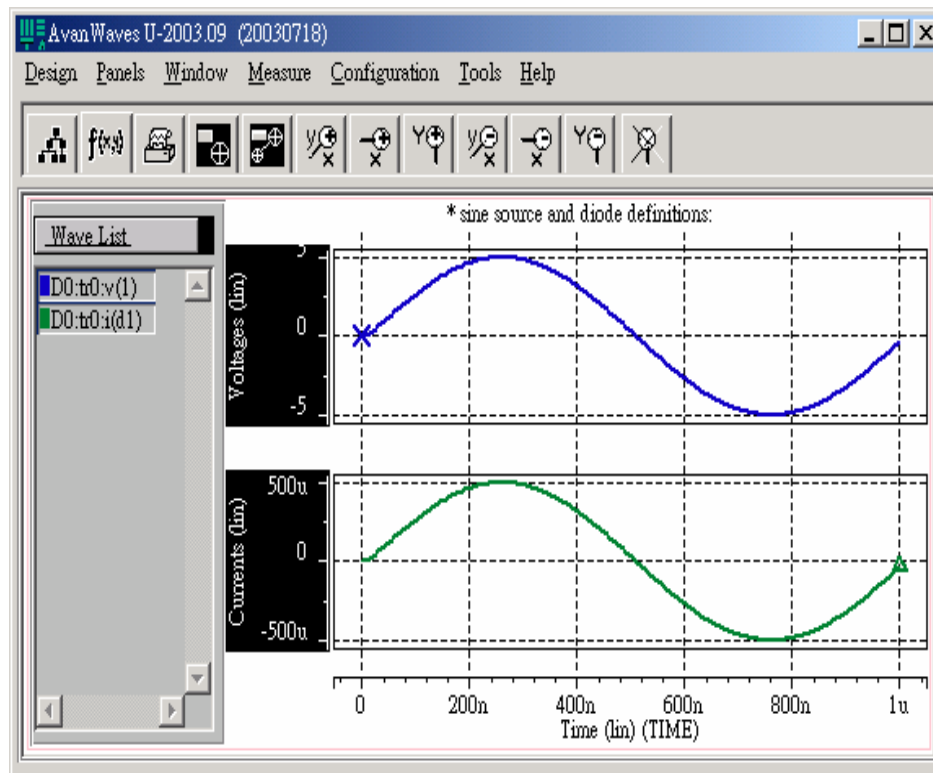

mos_pwl.sp

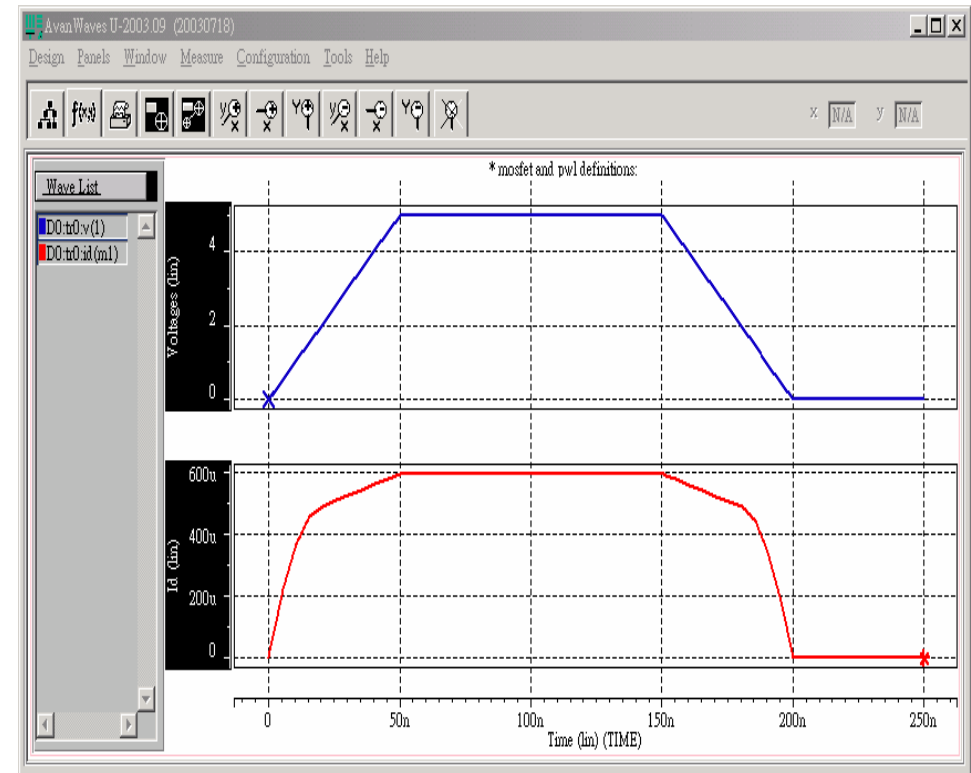



Chapter 5

Analysis Types



Analysis Types & Orders

● Types & Order of Execution :

- DC Operating Point : *First Calculated for ALL Analysis Types*

.OP **.IC** **.NODESET**

- DC Sweep & DC Small Signal Analysis :

.DC **.TF** **.PZ** **.SENS**

- AC Sweep & Small Signal Analysis :

.AC **.NOISE** **.DISTO** **.SAMPLE** **.NET**

- Transient Analysis:

.TRAN **.FOUR** **(UIC)** **.FFT**

● Other Advanced Modifiers :

- Temperature Analysis, **Optimization**



DC Operating Point Analysis

● Initialization and Analysis:

- First Thing to Set the DC Operating Point Values for All Nodes and Sources : Set Capacitors **OPEN** & Inductors **SHORT**
- Using **.IC** or **.NODESET** to set the Initialized Calculation
- If **UIC** Included in **.TRAN** ==> Transient Analysis **Started Directly** by Using Node Voltages Specified in **.IC** Statement
- **.NODESET** Often Used to Correct Convergence Problems in **.DC** Analysis
- **.IC** force DC solutions, however **.NODESET** set the initial guess

● **.OP** Statement :

- **.OP** Print out :(1). Node Voltages; (2). Source Currents; (3). Power Dissipation; (4). Semiconductors Device Currents, Conductance, Capacitance



DC Sweep & DC Small Signal Analysis

● DC Analysis Statements :

- **.DC** : Sweep for Power Supply, Temp., Param., & Transfer Curves
- **.OP** : Specify Time(s) at which **Operating Point** is to be Calculated
- **.TF** : Calculate DC Small-Signal Transfer Function (.OP is not Required)
- **.PZ** : Performs Pole/Zero Analysis (.OP is not Required)
- **.SENS** : Performs DC Small-Signal Sensitivities. (.OP is not Required)

● .DC Statement Sweep :

- Any Source Value
- **Temperature** Value
- DC Circuit **Optimization**
- Any Parameter Value
- DC Model Characterization
- DC Monte Carlo(Random Sweep)

Sweep over model parameter is not allowed

Monte Carlo sweep is not supported in SBTSPICE



DC Sweep & DC Small Signal Analysis (Cont.)

● .DC Analysis : Syntax

```
.DC var1 start1 stop1 incr1 < var2 start2 stop2 incr2 > )
```

```
.DC var1 start1 stop1 incr1 < SWEEP var2 DEC/OCT/LIN/POI np start2 stop2 > )
```

● Examples :

```
.DC VIN 0.25 5.0 0.25
```

```
.DC VDS 0 10 0.5 VGS 0 5 1
```

```
.DC TEMP -55 125 10
```

```
.DC TEMP POI 5 0 30 50 100 125
```

```
.DC xval 1k 10k 0.5k SWEEP TEMP LIN 5 25 125
```

```
.DC DATA=datanm SWEEP par1 DEC 10 1k 100k
```

```
.DC par1 DEC 10 1k 100k SWEEP DATA=datanm
```





DC Sweep & DC Small Signal Analysis (Cont.)

● Examples :

```
*** DC sweep example  
m1 out in 0 0 nch l=1u w=1u  
r1 vdd out 100k  
vdd vdd 0 5  
vin in 0  
.model nch nmos level=2
```

```
.DC vin 0 5 0.5
```

```
.option post  
.end
```

  




DC Sweep & DC Small Signal Analysis (Cont.)

```
*** DC sweep example
m1 vd vg vs 0 nch l=1u w=10u
*** mos model
.model nch nmos level=2
*** voltage
vds vd vs
vgs vg vs

.DC VDS 0 5 0.5 VGS 0 5 1



.probe dc i(m1)
.end
```

 



DC Sweep & DC Small Signal Analysis (Cont.)
  
```
*** DC sweep example
m1 out in 0 0 nch l=1u w=1u
r1 vdd out 150k
vdd vdd 0 5
vin in 0
.model nch nmos level=2
.DC vin 0 5 0.1 SWEEP TEMP POI 6 -100 -50 0 50 100 125
.option post
.end
```





DC Sweep & DC Small Signal Analysis (Cont.)

- **Transfer function** statement

```
.TF V(OUT) VIN    **output-variable, input-source
```

****NOTE: Compute Transfer Function $v(\text{out})/v_{\text{in}}$, R_{in} , R_{out}**

- **Example:**

```
*** tf example
.subckt inv in out
mn1 out in vss! vss! nch l=1u w=10u
mp1 out in vdd! vdd! pch l=1u w=20u
.ends
.model nch nmos level=1
.model pch pmos level=1
```

```
x1 in out inv
.global vdd! vss!
vdd! vdd! 0 5
vss! vss! 0 0
vin in 0
.tf v(out) vin
.end
```

```
**** small-signal transfer characteristics
v(out)/vin           = -2.4582n
input resistance at vin = 1.000e+20
output resistance at v(out) = 1.1902k
```



DC Sweep & DC Small Signal Analysis (Cont.)

- Pole/Zero statement

```
.PZ V(OUT) VIN **output-variable, input-source
```

****NOTE: Complete information about pole/zero analysis**

```
***** pole/zero analysis tnom= 25.000 temp= 25.000
```

```
....
```

```
poles (rad/sec)          poles ( hertz)
```

```
*****
```

real	imag	real	imag
-1.0393x	0.	-165.4096k	0.
-12.7888g	0.	-2.0354g	0.

```
.....
```

```
zeros (rad/sec)         zeros ( hertz)
```

```
*****
```

real	imag	real	imag
-12.7834g	0.	-2.0345g	0.
-45.4697g	20.0122g	-7.2367g	3.1850g



DC Sweep & DC Small Signal Analysis (Cont.)

- Pole/Zero Example:

```
** differential amp
.subckt dopa va vb out
M1 net1 va net2 0 nch w=25u l=1u
M2 out vb net2 0 nch w=25u l=1u
M3 net1 net1 vdd! vdd! pch w=8u l=1u
M4 out net1 vdd! vdd! pch w=8u l=1u
M5 net2 net3 0 0 nch w=123u l=1u
M6 net3 net3 vdd! vdd! pch w=1u l=1u
M7 net3 net3 0 0 nch w=100u l=1u
Cl out 0 5p
.ends
.model nch nmos level=2
.model pch pmos level=2
```

```
** supply voltage
.GLOBAL vdd! vss!
vdd vdd! 0 3.3
vss vss! 0 0
xopa1 ina inb out dopa
vr1 inb 0 dc 1.65
vin ina inb ac 1.65 ** input signal
.option post
.pz v(out) vin
.end
```



DC Sweep & DC Small Signal Analysis (Cont.)

- **Sensitivity** statement

```
.SENS V(OUT) I(VCC) **branch currents or nodal voltage for DC component  
**sensitivity analysis
```

****NOTE: Generate very large amounts of output for large circuits**

* .sens example

```
r1 1 2 1  
r2 2 0 2  
r3 2 3 3  
r4 3 0 4  
vin 1 0 10
```

```
.sens v(3)
```

```
.end
```

*obtains the dc small-signal sensitivities of

***** **dc sensitivity analysis**



dc sensitivities of output v(3)

element name	element value	element sensitivity (volts/unit)	normalized sensitivity (volts/percent)
0:r1	1.0000	-1.3611	-13.6106m
0:r2	2.0000	529.3006m	10.5860m
0:r3	3.0000	-453.6862m	-13.6106m
0:r4	4.0000	415.8790m	16.6352m
0:vin	10.0000	347.8261m	34.7826m
0:r4:i1	0.	478.2609m	0.



Floating – Diode Limiter

 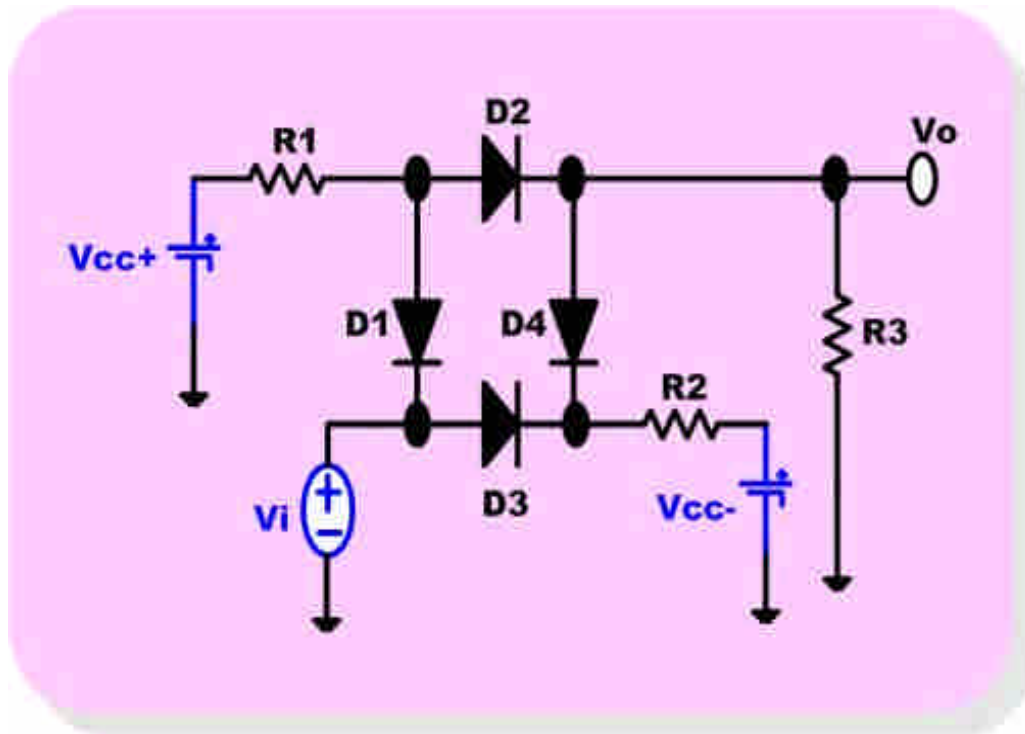***error* only 1 connection at node 0:net5 defined in subckt 0**





AC Sweep & Small Signal Analysis

● AC Analysis Statements :

- **.AC** : Calculate Frequency-Domain Response
- **.NOISE** : Noise Analysis
- **.DISTO** : Distortion Analysis
- **.SAMPLE** : Sampling Noise Analysis
- **.NET** : Network Analysis

● .AC Statement Sweep :

- | | |
|----------------|-------------------------------------|
| ■ Frequency | ■ Element |
| ■ Temperature | ■ .param Parameter |
| ■ Optimization | ■ Monte Carlo(Random Distribution) |



AC Sweep & Small Signal Analysis(Cont.)

● .AC Analysis : Syntax

```
.AC DEC/OCT/LIN/POI np fstart fstop
```

```
.AC DEC/OCT/LIN/POI np fstart fstop < SWEEP var start stop incr > )
```

● Examples :

```
.AC DEC 10 1K 100MEG
```

```
.AC LIN 100 1 100Hz
```

```
.AC DEC 10 1 10K SWEEP Cload LIN 20 1pf 10pf
```

```
.AC DEC 10 1 10K SWEEP Rx POI 2 5K 15K
```

```
.AC DEC 10 1 10K SWEEP DATA=datanm
```




AC Sweep & Small Signal Analysis(Cont.)

```

** differential amp
.subckt dopa va vb out
M1 net1 va net2 0 nch w=25u l=1u
M2 out vb net2 0 nch w=25u l=1u
M3 net1 net1 vdd! vdd! pch w=8u l=1u
M4 out net1 vdd! vdd! pch w=8u l=1u
M5 net2 net3 0 0 nch w=123u l=1u
M6 net3 net3 vdd! vdd! pch w=1u l=1u
M7 net3 net3 0 0 nch w=100u l=1u
Cl out 0 5p
.ends
.model nch nmos level=2
.model pch pmos level=2
.GLOBAL vdd! vss!
vdd vdd! 0 3.3
vss vss! 0 0
xopa1 ina inb out dopa
vr1 inb 0 dc 1.65
  
```

```

 vin ina inb ac 1.65 ** input signal
.ac dec 10 1k 100meg
.probe vdb(out)
.option post
.end
  
```





AC Sweep & Small Signal Analysis(Cont.)

- **Other AC Analysis Statements:**

- **.NOISE** Statement : **Only one noise analysis per simulation**

```
.NOISE v(5) VIN 10      $ output-variable, noise-input reference, interval
```

V(5) <- node output at which the noise output is summed

VIN <- noise input reference node

10 <- interval at which noise analysis summary is to be printed



Transient Analysis

● Transient Analysis Statements :

- **.TRAN** : Calculate Time-Domain Response
- **.FOUR** : Fourier Analysis
- **.FFT** : Fast Fourier Transform

● .TRAN Statement Sweep :

- **Temperature**
- **Optimization**
- **.Param Parameter**
- **Monte Carlo (Random Distribution)**



Transient Analysis (Cont.)

- **.TRAN Analysis : Syntax**

```
.TRAN tincr1 tstop1 < tincr2 tstop2 ..... > < START=val>
```

```
.TRAN tincr1 tstop1 < tincr2 tstop2 ..... > < START=val> UIC <SWEEP..>
```

- **Examples :**

```
.TRAN 1NS 100NS
```

```
.TRAN 10NS 1US UIC
```

```
.TRAN 10NS 1US UIC SWEEP TEMP -55 75 10 $ step=10
```

```
.TRAN 10NS 1US SWEEP load POI 3 1pf 5pf 10pf
```

```
.TRAN DATA=datanm
```




Transient Analysis (Cont.)

```
** differential amp
.subckt dopa va vb out
M1 net1 va net2 0 nch w=25u l=1u
M2 out vb net2 0 nch w=25u l=1u
M3 net1 net1 vdd! vdd! pch w=8u l=1u
M4 out net1 vdd! vdd! pch w=8u l=1u
M5 net2 net3 0 0 nch w=123u l=1u
M6 net3 net3 vdd! vdd! pch w=1u l=1u
M7 net3 net3 0 0 nch w=100u l=1u
Cl out 0 5p
.ends
.model nch nmos level=2
.model pch pmos level=2
.GLOBAL vdd! vss!
vdd vdd! 0 3.3
vss vss! 0 0
xopa2 ina2 out2 out2 dopa
vin2 ina2 0 pwl (0 0 10n 0 100n 3.3 510n 3.3 600n 0)
```



Transient Analysis (Cont.)
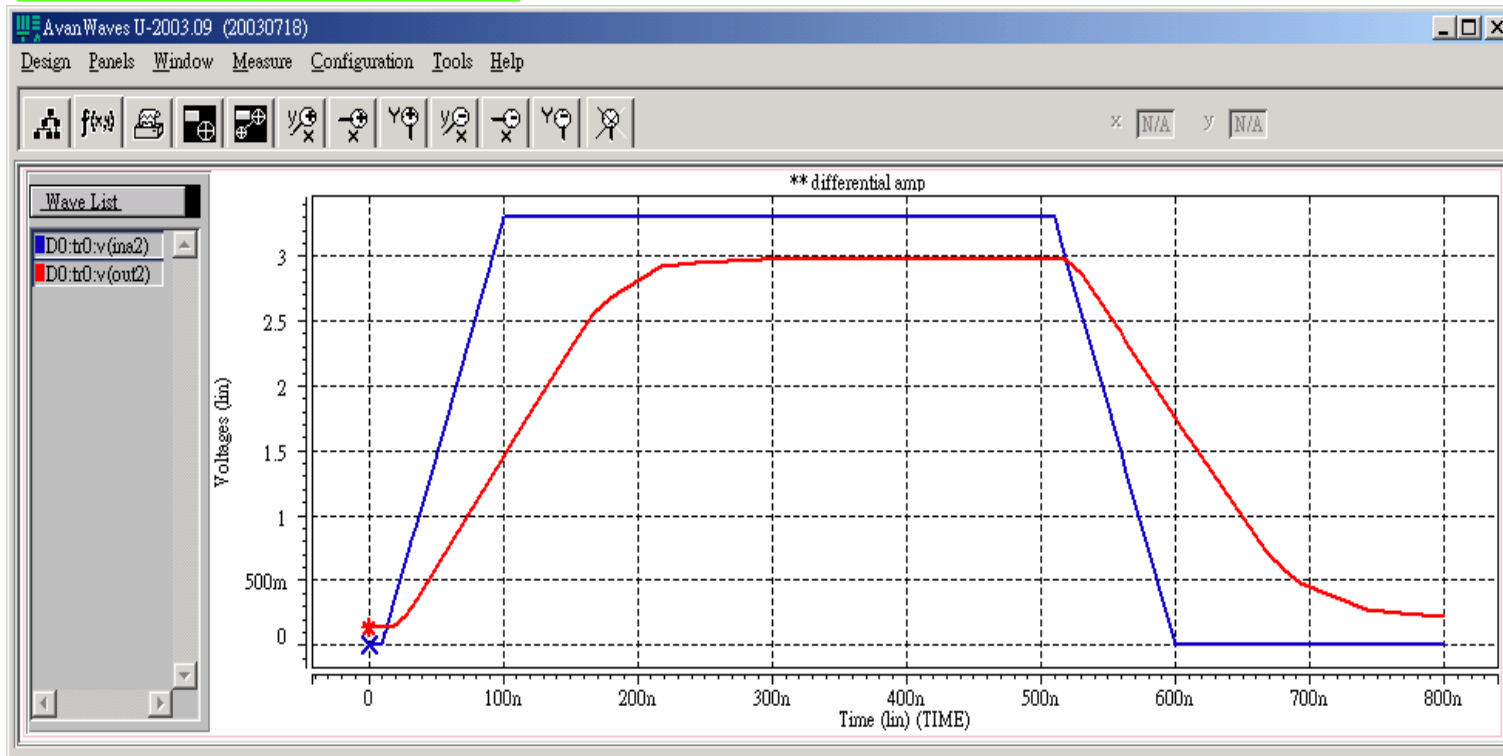
```
.tran 10n 800n  
.option post  
.end
```





Transient Analysis (Cont.)

● Other Transient Analysis Statements:

■ .FOUR Statement :

.FOUR freq ov1 \$ fundamental-freq , output-variable1,2,.....

Note1: As a part of Transient Analysis

*Note2: Determines DC and first **Nine** AC Harmonics & Reports THD (%)*

*** fourier series example

vin in 0 pulse (-2 2

+ 0 10n 10n 0.1m 0.2m)


r1 in out 100k

c1 out 0 1n

.tran 1u .2m

.four 5k v(out)

.end

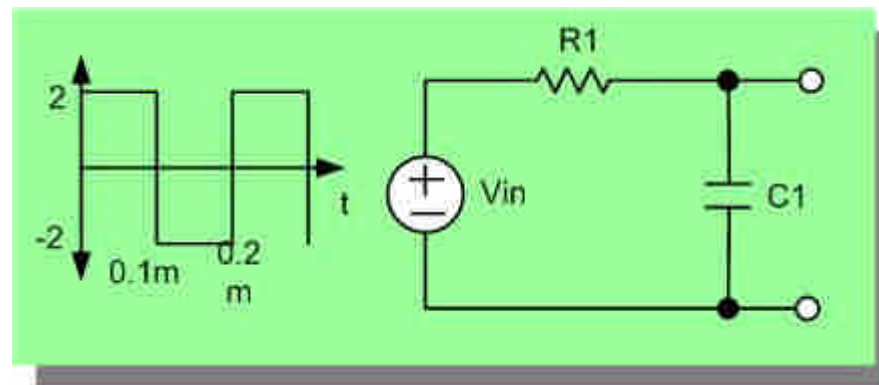

$$\text{THD} = \frac{1}{R1} \cdot \left(\sum_{m=2}^9 R_m^2 \right)^{1/2} \cdot 100\%$$



Transient Analysis (Cont.)

fourier components of transient response v(out)

dc component = -4.658D-01

harmonic no	frequency (hz)	fourier component	normalized component	normalized phase (deg)	normalized phase (deg)
1	5.0000k	824.3853m	1.0000	-92.4135	0.
2	10.0000k	146.4523m	177.6503m	-170.2336	-77.8200
3	15.0000k	134.3362m	162.9531m	-131.0504	-38.6368
4	20.0000k	73.9205m	89.6674m	-174.0062	-81.5927
5	25.0000k	68.4249m	83.0011m	-146.3467	-53.9332
6	30.0000k	49.3735m	59.8912m	-174.7982	-82.3847
7	35.0000k	46.1717m	56.0074m	-153.9257	-61.5122
8	40.0000k	37.0599m	44.9546m	-174.8353	-82.4217
9	45.0000k	35.0115m	42.4698m	-158.1674	-65.7538

total harmonic distortion = 28.9121 percent



Transient Analysis (Cont.)


■ .FFT Statement :

.FFT v(1,2) np=1024 start=0.3m stop=0.5m freq=5K window=Hamm alfa=2.5

Note1: Window Types : RECT, BLACK, HAMM, GAUSS, KAISER, HINN...

*Note2: Determines DC and first **Ten** AC Harmonics & Reports THD (%)*
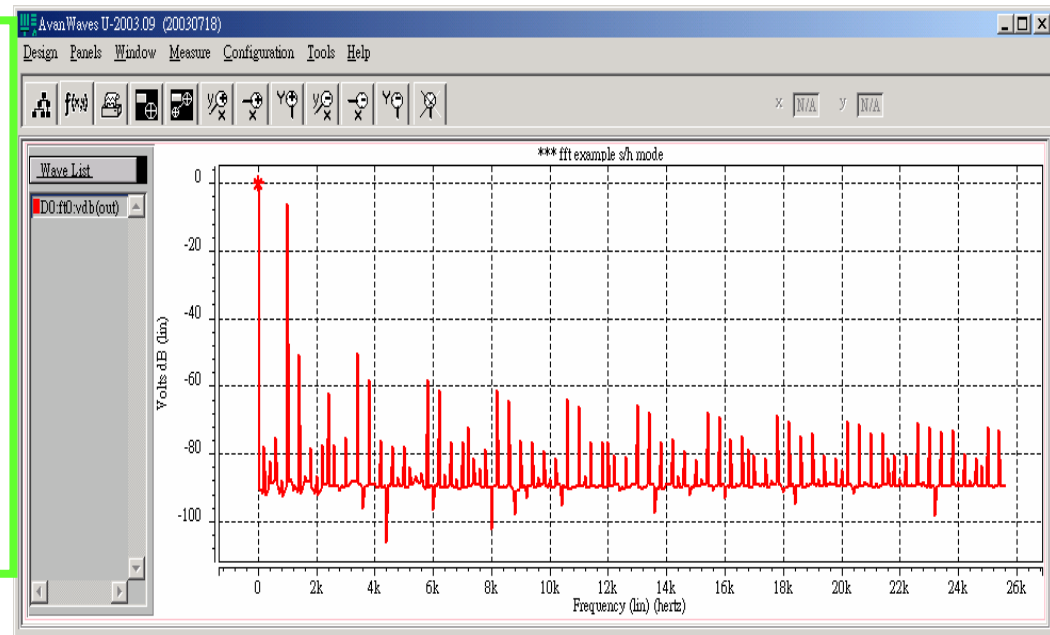
```
*** fft example s/h mode
m1 out clk in vss! nch l=1u w=5u
c1 out 0 1p
vin in 0 sin(1 1 1k)
vclk clk 0 pulse(0 5 0 1n 1n 5u 10u)
.model nch nmos level=2
.fft v(out) 1k 1024
.tran 10u 20m
.option post
.end
```





Transient Analysis (Cont.)

fft components of transient response v(out)

Window: Rectangular

DC: ON

First Harmonic: 1.0000k

Start Freq: 1.0000k

Stop Freq: 25.6000k

dc component: mag(db)= 0.000D+00 mag= 1.000D+00 phase= 0.000D+00

frequency frequency fft_mag fft_mag fft_phase


index	frequency (hz)	fft_mag (db)	fft_mag (deg)	fft_phase
20	1.0000k	-6.0077	500.7442m	-90.4639
40	2.0000k	-86.5629	46.9737u	-37.4189
60	3.0000k	-75.0164	177.4933u	119.2220
80	4.0000k	-88.6074	37.1217u	15.4612
100	5.0000k	-77.5812	132.1107u	132.7042
120	6.0000k	-96.4409	15.0644u	-1.6789
.....				
480	24.0000k	-88.2746	38.5718u	8.0802
500	25.0000k	-72.0603	249.4506u	110.3186

total harmonic distortion = 187.3653m percent



Lab4 Differential Amplifier

- **Differential Amplifier Circuit** - .ac type analysis
- **Observe AV , GB , PM**

 



Chapter 6

Simulation Output and Controls



Output Files Summary (HSPICE):

Output File Type	Extensi
Output Lis	.lis
DC Analysis Results	.sw#
DC Analysis Measurement Results	.ms#
AC Analysis Results	.ac#
AC Analysis Measurement Results	.ma#
Transient Analysis Results	.tr#
Transient Analysis Measurement Results	.mt#
Subcircuit Cross-Listing	.pa#
Operating Point Node Voltages (Initial Condition)	.ic



Output Statements

● Output Commands :

- **.PRINT Statement** : Print Numeric Analysis Results
- **.PLOT Statement** : Generates Low Resolution Plot in .lis file
- **.PROBE Statement** : Allows Save Output Variables Only into the Graph Date Files
- **.MEASURE Statement** : Print Numeric Results of Measured Specifications

● Output Variables:

- **DC and Transient Analysis** : Displays Individual Voltage, Current, & Power
- **AC Analysis** : Display Real & Imag. Components of Voltage & Current.....
- **Element Template Analysis** : Display Element-Specific Voltage, Current.....
- **.MEASURE** : Display User-Defined Variables Defined in .MEAS Statement



Output Variable Examples

● DC & Transient Analysis :

- Nodal Voltage Output : $V(1)$, $V(3,4)$, $V(X3.5)$
- Current Output (Voltage Source) : $I(VIN)$, $I(X1.VSRC)$
- Current Output (Element Branches) : $I2(R1)$, $I1(M1)$, $I4(X1.M3)$

● AC Analysis :

- AC : $V(2)$, $VI(3)$, $VM(5,7)$, $VDB(OUT)$, $IP(9)$, $IP4(M4)$

● Element Template :

- $mn1[vth] \rightarrow LV9(mn1)$
- $mn1[gds] \rightarrow LX8(mn1)$
- $mn1[gm] \rightarrow LX7(mn1)$
- $mn1 \text{ gate caps (cgs+cgd+cgb)} \rightarrow LX18(mn1)$

R : Real
I : Imaginary
M : Magnitude
P : Phase
DB : Decibels



Parametric Statements

● Algebraic Expressions for Output Statements:

- `.PRINT DC V(IN) V(OUT) PAR('V(OUT)/V(IN)')`
- `.PROBE AC Gain=PAR('VDB(5)-VDB(2)') Phase=PAR('VP(5)-VP(2)')`

● Other Algebraic Expressions :

- Parameterization : `.PARAM WN=5u LN=10u VDD=5.0V`
- Algebra : `.PARAM X='Y+5'`
- Functions : `.PARAM Gain(IN, OUT)='V(OUT)/V(IN)'`
- Algebra in Element : `R1 1 0 r='ABS(V(1)/I(M1))+10'`

● Built-In Functions :

`sin(x) cos(x) tan(x) asin(x) acos(x) atan(x) sinh(x) tanh(x) abs(x)`
`sqrt(x) log(x) log10(x) exp(x) db(x) min(x,y) max(x,y) power(x,y)...`

Ex: `.print tran Gain=PAR('log (V(out)/V(in)) ')`



.PRINT & .PLOT

● Syntax :

.PRINT anatype ov1 <ov2 ov2...>

*Note : .PLOT with same Syntax as .PRINT, Except Adding <pol1, phi1>
to set plot limit*

● Examples :

.PRINT TRAN V(4) V(X3.3) P(M1) P(VIN) POWER PAR('V(OUT)/V(IN)')

.PRINT AC VM(4,2) VP(6) VDB(3)

.PRINT AC INOISE ONOISE VM(OUT) HD3

.PRINT DISTO HD3 HD3(R) SIM2

.PLOT DC V(2) I(VSRC) V(37,29) I1(M7) BETA=PAR('I1(Q1)/I2(Q1)')

.PLOT AC ZIN YOUT(P) S11(DB) S12(M) Z11(R)

.PLOT TRAN V(5,3) (2,5) V(8) I(VIN)



.PROBE & .GRAPH

● .PROBE Statement :

.PROBE Syntax : .PROBE anatype ov1 <ov2 ov2...>

Note 1 : .PROBE Statement Saves Output Variables into the Interface & Graph Data Files

*Note 2 : Set **.OPTION PROBE** to Save Output Variables **Only**, Otherwise HSPICE Usually Save All Voltages & Supply Currents in Addition to Output Variables*

*Note 3 : Set **.OPTION POST** to save data into the **Graph Data Files***



MEASURE Statement

● General Descriptions :

- **.MEASURE** Statement Prints User-Defined Electrical Specifications of a Circuit and is Used Extensively in **Optimization**
- **.MEASURE** Statement Provides Oscilloscope-Like Measurement Capability for either AC , DC, or Transient Analysis
- Using **.OPTION AUTOSTOP** to Save Simulation Time when **TRIG-TARG** or **FIND-WHEN** Measure Functions are Calculated

● Fundamental Measurement Modes :

- **Rise, Fall, and Delay (TRIG-TARG)**
- **AVG, RMS, MIN, MAX, & Peak-to-Peak (FROM-TO)**
- **FIND-WHEN**



MEASURE : Rise, Fall, and Delay

- **Syntax :** 畫個時序圖(pulse waveform), 來說明measure capability

```
.MEASURE DC|AC|TRAN result_var TRIG ... TARG ... <Optimization Option>
```

- **result_var** : Name Given the Measured Value in HSPICE Output
 - **TRIG ...** : **TRIG** *trig_var* VAL=*trig_value* <TD=*time_delay*> <CROSS=*n*>
+ <RISE=*r_n*> <FALL=*f_n*/LAST>
 - **TRIG ...** : **TRIG** AT=*value*
 - **TARG ...** : **TARG** *targ_var* VAL=*targ_value* <TD=*time_delay*>
+ <CROSS=*n*/LAST> <RISE=*r_n*/LAST> <FALL=*f_n*/LAST>
 - <Optimization Option> : <GOAL=*val*> <MINVAL=*val*> <WEIGHT=*val*>
- **Example:**

```
.meas TRAN tprop trig v(in) val=2.5 rise=1 targ v(out) val=2.5 fall=1
```



MEASURE : AVG, RMS, MIN, MAX, & P-P

● Syntax :

```
.MEASURE DC/AC/TRAN result FUNC out_var <FROM=val1> <TO=val2>  
+ <Optimization Option>
```

- **result_var** : Name Given the Measured Value in HSPICE Output
- **FUNC** : **AVG** ----- Average **MAX** ----- Maximun **PP** ---- Peak-to-Peak
 MIN ----- Minimum **RMS** ----- Root Mean Square
- **out_var** : Name of the Output Variable to be Measured
- **<Optimization Option>**: **<GOAL=val>** **<MINVAL=val>** **<WEIGHT=val>**

● Example:

```
.meas TRAN minval        MIN v(1,2)    from=25ns to=50ns  
.meas TRAN tot_power    AVG power    from=25ns to=50ns  
.meas TRAN rms_power    RMS power
```



MEASURE : *Find & When Function*

● Syntax :

```
.measure DC|AC|TRAN result WHEN ... <Optimization Option>  
.measure DC|AC|TRAN result FIND out_var1 WHEN ...<Optimization Option>  
.measure DC|AC|TRAN result_var FIND out_var1 AT=val <Optimization Option>
```

- **result** : Name Given the Measured Value in HSPICE Output
- **WHEN ...** : **WHEN** out_var2=val/out_var3 <TD=time_delay>
+ <CROSS=n/LAST> <RISE=r_n/LAST> <FALL=f_n/LAST>
- <Optimization Option> : <GOAL=val> <MINVAL=val> <WEIGHT=val>

● Example:

```
.meas TRAN fifth WHEN v(osc_out)=2.5V rise=5  
.meas TRAN result FIND v(out) WHEN v(in)=2.5V rise=1  
.meas TRAN vmin FIND v(out) AT=30ns
```




MEASURE : Application Examples

● Rise, Fall, and Delay Calculations :

```

 .meas TRAN Vmax MAX v(out) FROM=TDval TO=Tstop
.meas TRAN Vmin MIN v(out) FROM =TDval TO =Tstop
.meas TRAN Trise TRIG v(out) VAL='Vmin+0.1*Vmax' TD=TDval RISE=1
+ TARG v(out) VAL='0.9*Vmax' RISE=1
.meas TRAN Tfall TRIG v(out) VAL='0.9*Vmax' TD=TDval FALL=2
+ TARG v(out) VAL='Vmin+0.1*Vmax' FALL=2
.meas TRAN Tdelay TRIG v(in) VAL=2.5 TD=TDval FALL=2
+ TARG v(out) VAL=2.5 FALL=2
    
```






MEASURE : Application Examples(Cont.)

● Ripple Calculation :
 
```
.meas TRAN Th1 WHEN v(out)='0.5*v(Vdd)' CROSS=1
.meas TRAN Th2 WHEN v(out)='0.5*v(Vdd)' CROSS=2
.meas TRAN Tmid PARAM='(Th1+Th2)/2'
.meas TRAN Vmid FIND v(out) AT='Tmid'
.meas TRAN Tfrom WHEN v(out)='Vmid' RISE=1
.meas TRAN Ripple PP v(out) FROM='Tfrom' TO='Tmid'
```





MEASURE : Application Examples(Cont.)

● Unity-gain Freq, Phase margin, & DC gain(db/M):


```
.meas AC unitfreq    WHEN vdb(out)=0    FALL=1
.meas AC phase      FIND  vp(out)      WHEN vdb(out)=0
.meas AC 'gain(db)'  MAX    vdb(out)
.meas AC 'gain(mag)' MAX    vm(out)
```

● Bandwidth & Quality Factor (Q):

```
.meas AC gainmax    MAX    vdb(out)
.meas AC fmax       WHEN  vdb(out)='gainmax'
.meas AC band       TRIG  vdb(out)  VAL='gainmax-3.0'  RISE=1
+                   TARG  vdb(out)  VAL='gainmax-3.0'  FALL=1
.meas AC Q_factor   PARAM='fmax/band'
```



Lab5 Buffer & High Q Bandpass Filters

 



Chapter 7

Elements and Device Models



Types of Elements

● Passive Devices :

- *R* ---- Resistor
- *C* ---- Capacitor
- *L* ---- Inductor
- *K* ---- Mutual Inductor

● Active Devices :

- *D* ---- Diode
- *Q* ---- BJT
- *J* ---- JFET and MESFET
- ★ ■ *M* ---- MOSFET

● Other Devices :

- Subcircuit (*X*)
- Behavioral (*E,G,H,F,B*)
- Transmission Lines (*T,U,O*)



R, C, L, and K Elements

● Passive Devices Parameters :

	Resistor	Capacitor	Inductor	Mutual Inductor
Netlist	Rxxx, n1,n2, mname, rval	Cxxx, n1,n2, mname, cval	Lxxx, n1,n2, mname, lval	Kxxx, Lyyy, Lzzz, kval
Temperature	DTEMP, TC1, TC2	DTEMP, TC1, TC2	DTEMP, TC1, TC2	
Geometric	L, M, W, SCALE	L, M, W, SCALE	M, SCALE	
Parasitics	C		R	
Initialization		IC(v)	IC(i)	

● Examples :

```

R1 12 17 1K TC1=1.3e-3 TC2=-3.1e-7
C2 7 8 0.6pf IC=5V
LSHUNT 23 51 10UH 0.01 1 IC=15.7mA
K4 Laa Lbb 0.9999
    
```



Diodes

TYPE	Parameters
Netlist	Dxxx, n+, n-, mname
Temperature	DTEMP
Geometric	AREA, L, W, PJ, M
Initialization	IC, OFF

- **Syntax Examples :**

D1 n1 n2 diode AREA=1.5 IC=0.6

- **Model Syntax:**

.MODEL mname D <param=val>.....

- **Models:**

Level 1 nongeometric junction model – no SCALM

Level 2 Fowler-Nordheim model – M (Insulator)S device

Level 3 geometry junction model ** Foundry supplied



BJT Element

- **BJT Element Parameters :**

TYPE	Parameters
Netlist	Qxxx, nc, nb, ne, ns, mname
Temperature	DTEMP
Geometric	AREA, AREAB, AREAC, M
Initialization	IC(VBE, VCE), OFF

- **BJT Syntax Examples :**

```
Q100 NC NB NE QPNP AREA=1.5 AREAB=2.5 AREAC=3.0 IC= 0.6, 5.0
```

- **BJT Model Syntax :**

```
.MODEL mname NPN (PNP) <param=val> .....
```

- **BJT Models in SBTSPICE:** *Gummel-Poon Model*



MOSFET Element

● MOSFET Element Syntax :

```
Mxxx nd ng ns <nb> mname <L=val> <W=val> <AD=val> <AS=val>  
+ <PD=val> <PS=val> <NRD=val>  
+ <NRS=val>  
+ <OFF> <IC=vds,vgs,vbs> <M=val>  
+ <TEMP=val> <GEO=val> <DELVTO=val>
```

● MOSFET Element Statement Examples:

```
M1 24 2 0 20 MODN L=5u W=100u M=4  
M2 1 2 3 4 MODN 5u 100u  
M3 4 5 6 8 N L=2u W=10u AS=100P AD=100p PS=40u PD=40u
```

```
.OPTIONS SCALE=1e-6  
M1 24 2 0 20 MODN L=5 W=100 M=4
```



MOSFET Introduction

● MOSFET Model Overview :

- MOSFET Defined by : (1). MOSFET Model & Element Parameters
(2). Two Submodel : **CAPOP** & **ACM**
- **CAPOP** : Specifies MOSFET Gate Capacitance
- **ACM** : Modeling of MOSFET **Bulk_Source** & **Bulk_Drain** Diodes

● MOSFET Model Levels :

- Available : **All the public domain spice model**
- Level = 4 or 13 : **BSIM1**
- **Modified BSIM1**
- Level = 5 or 39 : **BSIM2**
- **Level = 49/53 : BSIM3V3 ,53 for Berkeley BSIM3 code**
- **Level = 8 : SBT MOS8**
- **Level = 54 BSIM4**



Model Statement

● MOSFET Model Syntax :

```
.MODEL mname NMOS <LEVEL=val> <name1=val1> <name2=val2>.....  
.MODEL mname PMOS <LEVEL=val> <name1=val1> <name2=val2>.....
```

● MOSFET Model Statement Examples:

```
.MODEL MODP PMOS LEVEL=2 VTO=-0.7 GAMMA=1.0.....  
.MODEL NCH NMOS LEVEL=39 TOX=2e-2 UO=600.....
```

● Corner_LIB of Models:

```
.LIB TT or (FF/SS/FS/SF)  
.param toxn=0.0141 toxp=0.0148.....  
.lib '~/.simulation/model/cmos.l' MOS  
.ENDL TT or (FF/SS/FS/SF)
```

```
.LIB MOS  
.MODEL NMOD NMOS (LEVEL=49  
+ TOXM=toxn LD=3.4e-8 , .....)  
.ENDL MOS
```



Automatic Model Selection


- **Automatic Model Selection :**

- HSPICE can Automatically Find the Proper Model for Each Transistor Size by Using Parameters, **LMIN,LMAX,WMIN, & WMAX** in MOSFET Models

```
.MODEL pch.4 PMOS WMIN=1.5u WMAX=3u LMIN=0.8u LMAX=2.0u
```

```
.MODEL pch.5 PMOS WMIN=1.5u WMAX=3u LMIN=2.0u LMAX=6.0u
```
 
```
M1 1 2 3 4 pch W=2u L=4u $ Automatically Select pch.5 Model
```






MOSFET Diode Model

- **MOSFET Diode Model : ACM**

- **Area calculation Method (ACM) Parameter** Allows for the Precise Control of Modeling **Bulk-Source & Bulk_Drain Diodes** within MOSFET Models

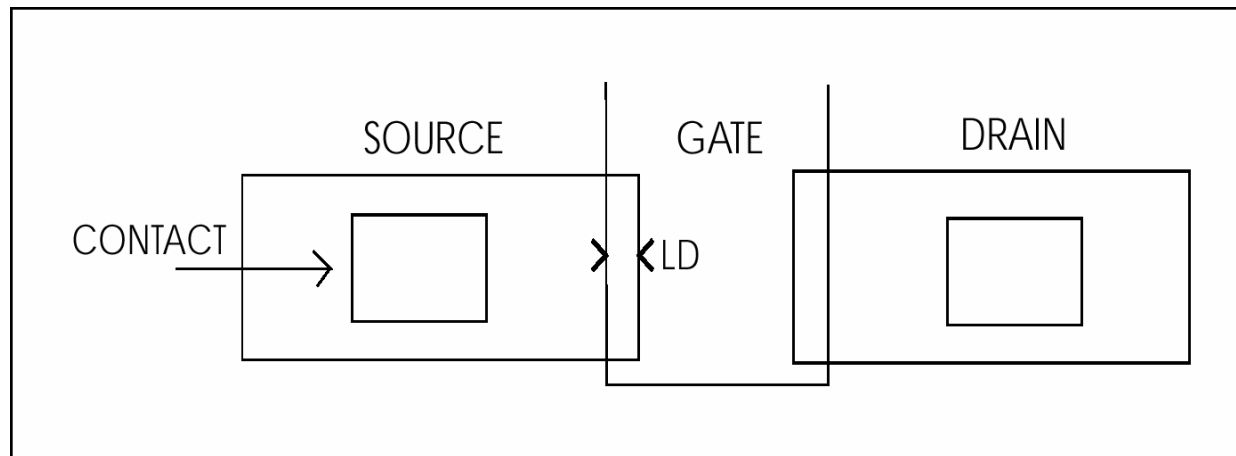- **ACM=0 MOSFET Diode: (Conventional MOSFET Structure)**




- **ACM=0** : PN Bulk Junction of MOSFET are Modeled in the SPICE-style.
- **ACM=0** : Not Permit Specifications of **HDIF & LDIF**.

$$A_{\text{Deff}} = M \cdot AD \cdot WMLT^2 \cdot SCALE^2$$



MOSFET Diode Model (Cont.)

● ACM=1 MOSFET Diode: (Not Popular)

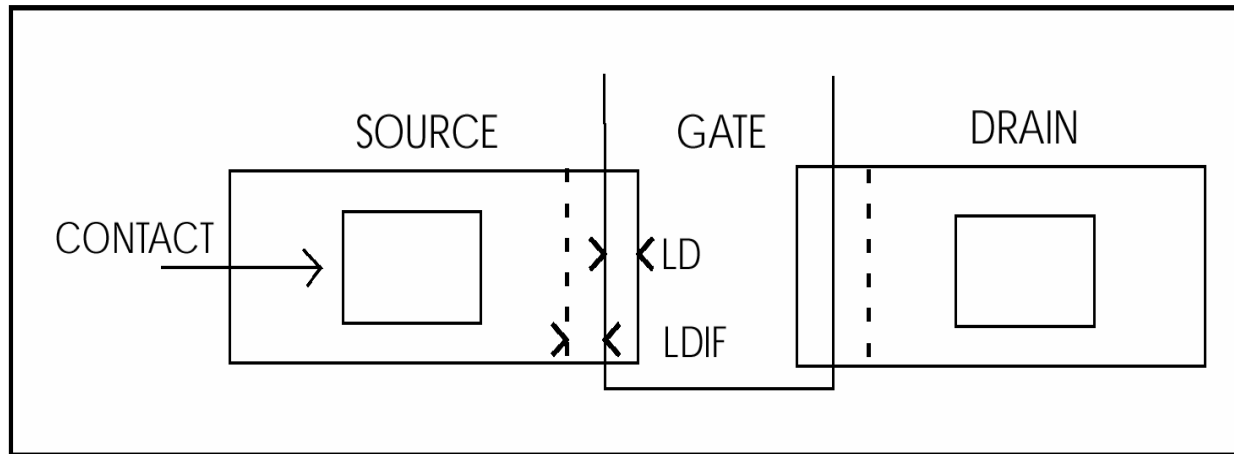


- **ACM=1** : **ASPEC-style** Diode Model.
- **ACM=1** : Parameter Function of Element **Width**.
- **ACM=1** : AS, AD, PS, & PD are not Used.
- **ACM=1** : JS and CJ Differ from the SPICE_style Diode (ACM=0)
Ignore AS,AD, PS,PD parameters

$$A_{Deff} = W_{eff} \cdot WMLT$$
$$P_{deff} = W_{eff}$$



MOSFET Diode Model (Cont.)

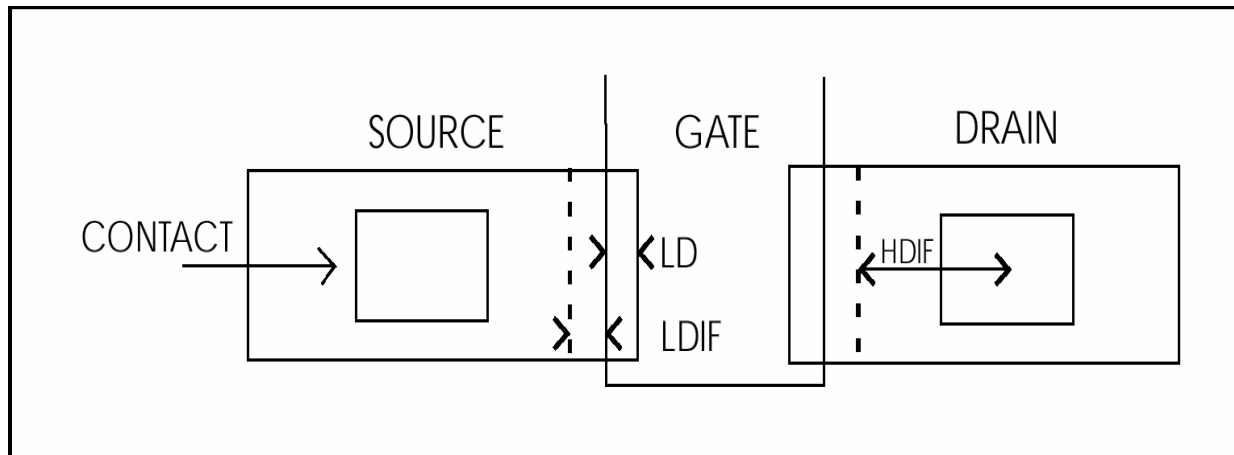● ACM=2 MOSFET Diode: (MOSFET LDD Structure)



- **ACM=2** : **HSPICE_Style** Diode Model, Combination of ACM=0 & 1.
- **ACM=2** : Supports both **Lightly & Heavily Doped Diffusions** by Settling LD, LDIF, and HDIF Parameters.
- **ACM=2** : Effective Areas and Peripheries can be Calculations by **LDIF & HDIF** (i.e. **AS, AD, PS, & PD can be Omitted in MOS Element Statement**)


$$A_{\text{Deff}} = 2 \cdot HDIF \cdot W_{\text{eff}}$$

$$P_{\text{Deff}} = 4 \cdot HDIF + 2 \cdot W_{\text{eff}}$$



MOSFET Diode Model (Cont.)

 - **ACM=3 MOSFET Diode** : (Stacked MOSFET Diode Model)



- **ACM=3** : Extension of ACM=2 Model that Deals with **Stacked Devices**.
- **ACM=3** : AS, AD, PS, & PD Calculations Depend on the Layout of the Device, which is Determined by the Value of Element Parameter **GEO**.
- **ACM=3** : **GEO=0 (Default)** Indicates Drain & source are not Shared by other Devices



Gate Capacitance Models

- **MOSFET Gate Capacitance Models:**

- Capacitance Model Parameters can be Used with all MOSFET Model Statement.
- Model Charge Storage Using Fixed and Nonlinear **Gate Capacitance** and **Junction Capacitance**.
- **Fixed Gate Capacitance** : Gate-to-Drain, Gate-to-Source, and Gate-to-Bulk Overlap Capacitances are Represented by **CGSO, CGDO, & CGBO**.
- **Nonlinear Gate Capacitance** : Voltage-Dependent MOS Gate Capacitance Depends on the Value of Model Parameter **CAPOP**.

- **MOSFET Gate Capacitance Selection :**

- Available CAPOP Values = 0, 1, **2(General Default)**, 4



Higher-Order Effects

- **Geometry and Doping Effects on V_{th} :**
 - Short Channel Effect (Small L)
 - Narrow Channel Effect (Small W)
 - Non-Uniform Doping Effect
- **Physical Effects on Output Resistance :**
 - Channel Length Modulation (CLM)
 - Drain Induced Barrier Lowering (DIBL)
 - Substrate Current Induced Body Effects (SCBE)
- **Other Physical Effects :**
 - Channel Mobility Degradation
 - Carrier Drift Velocity
 - Bulk Charge Effect
 - Parasitic Resistance
 - Subthreshold Current

Source : HP Eesof Device Modeling Seminar, March 1996



Historical Evolution

- **Can Define Three Clear Model “Generations”**
- **First Generation :**
 - “Physical” Analytical Models
 - Geometry Coded into the Model Equations
 - Level 1, Level 2, & Level 3
- **Second Generation :**
 - Shift in Emphasis to Circuit Simulation
 - Extensive Mathematical Conditioning
 - Individual Device Parameters & Separate Geometry Parameter
 - Shift “Action” to Parameter Extraction (Quality of Final Model is **Heavily** Dependent on Parameter Extraction)
 - **BSIM1, Modified BSIM1, BSIM2**

Source : IEEE 1997 CICC Educational Sessions E3.3



Historical Evolution (Cont.)

● Third Generation :

- “Original Intent” was a Return to **Simplicity**
- Scalable MOSFET model
- 1-st derivative is continuous
- Attempt to Re-Introduce a Physical Basis While Maintaining “Mathematical Fitness”
- **BSIM3, MOS-8, Other ???**

Source : IEEE 1997 CICC Educational Sessions E3.3



Overview of Most Popular MOSFET Models

- **UCB Level 1 : (Level = 1)**

- Shichman-Hodges Model (1968)
- Simple Physical Model, Applicable to $L > 10\mu\text{m}$ with Uniform Doping
- Not Precise Enough for Accurate Simulation
- Use only for Quick, Approximate Analysis of Circuit Performance

- **UCB Level 2 : (Level = 2)**

- Physical/Semi-Empirical Model
- Applicable to Long Channel Device ($\sim 10\ \mu\text{m}$)
- Advanced Version of Level 1 which Includes Additional Physical Effects
- Can Use either Electrical or Process Related Parameters

SPICE : Simulation Program with Integrated Circuit Emphasis

UCB : University of California at Berkeley



Overview of Most Popular MOSFET Models(Cont.)

- **UCB Level 3** : (Level = 3)

- Semi-Empirical Model Model (1979)
- Applicable to Long Channel Device (~ 2um)
- Includes Some New Physical Effects (DIBL, Mobility Degradation by Lateral Field)
- Very successful Model for Digital Design (Simple & Relatively Efficient)

- **BSIM** : (Level = 13)

- First of the “Second Generation” Model (1985)
- Applicable to Short Channel Device with $L \sim 1.0\mu\text{m}$
- Emphasis on Mathematical Conditioning of Circuit Simulation
- Empirical Approach to Small Geometry Effects

BSIM : Berkeley Short-Channel IGFET Model



Overview of Most Popular MOSFET Models (Cont.)

- **Modified BSIM1 LEVEL 28 :**

- Enhanced Version of BSIM 1, But Addressed most of the Noted Shortcomings
- Empirical Model Structure --> Heavy Reliance on Parameter Extraction for Final Model Quality
- Applicable to Deep Submicron Devices (~ 0.3 - 0.5um)
- Suitable for Analog Circuit Design

- **BSIM 2 : (HSPICE Level = 39)**

- “Upgraded” Version of BISM 1 (1990)
- Applicable to Devices with (L~ 0.2um)
- Drain Current Model has Better Accuracy and Better Convergence Behavior
- Covers the Device Physics of BSIM 1 and Adds Further Effects on Short Channel Devices



Overview of Most Popular MOSFET Models (Cont.)

- **BSIM 3v3** : (Level = 49)

- Newly Advanced Submicron MOSFET Model (Third Generation)
- Latest Physics-Based, **Deep-Submicron** Model (BSIM3v3.1)
- Use a **Single Equation** for a Device Property for All Regions of Device Operation, But Slow & Inefficient Behavior During Circuit Simulation
- Use of **Smoothing Functions** Greatly Improves Final Results
- Attempt to Impose “Global” Capability Creates a Number of Problems

In HSPICE, level=53 is BSIM 3V3 Berkeley compliance
 , level=49 is Avanti implemented BSIM3V3

- **MOS8 Model** : (SBTSPICE Level = 8)

- Developed by **SBT**
- 4-Terminals NQS charge-conservation model
- Physical-oriented scalable model



Overview of Most Popular MOSFET Models (Cont.)

● EKV Model :

- Developed at Swiss Federal Institute of Technology in Lausanne (EPFL)
- A Newly “Candidate” Model for Future Use
- Description of Small Geometry Effects is Currently Being Improved
- Developed for Low Power Analog Circuit Design
- Fresh Approach to FET Modeling
 - Use Substrate (not Source) as Reference
 - Simpler to Model FET as a Bi-Directional Element
 - Can Treat Pinch-Off and Weak Inversion as the same Physical Phenomenon
- First “Re-Thinking” of Analytical FET Modeling Since Early 1960s.

Source : IEEE 1997 CICC Educational Sessions E3.3



MOSFET Model Comparison

- **Model Equation Evaluation Criteria :** (Ref: HSPICE User Manual 1996, Vol._II)
 - Potential for Good Fit to Data
 - Ease of Fitting to Data
 - Robustness and Convergence Properties
 - Behavior Follows Actual Devices in All Circuit Conditions
 - Ability to Simulate Process Variation
 - Gate Capacitance Modeling
- **General Comments :**
 - Level 3 for Large Digital Design
 - HSPICE Level 28 for Detailed Analog/Low Power Digital
 - BSIM 3v3 & MOS Model 9 for Deep Submicron Devices
 - All While Keeping up with New Models

Source : IEEE 1997 CICC Educational Sessions E3.3



Chapter 8

Control Options & Convergence



Control Options : Output Format

- **Output Format : General (LIST, NODE, ACCT, OPTS, NOMOD)**
 - **.OPTION LIST** : Produces an Element Summary Listing of the Data to be Printed. (Useful in Diagnosing Topology Related **NonConvergence** Problems)
 - **.OPTION NODE** : Prints a Node Connection Table. (Useful in Diagnosing Topology Related **NonConvergence** Problems)
 - **.OPTION ACCT** : Reports Job Accounting and Run-Time Statistics at the End of Output Listing. (Useful in Observing **Simulation Efficient**)
 - **.OPTION OPTS** : Prints the Current Settings of All Control Options.
 - **.OPTION NOMOD** : Suppress the printout of Model Parameters (Useful in Decreasing **Size** of Simulation Listing Files)



Simulation Controls & Convergence

● Definition of “Convergence” :

- The Ability to Obtain a Solution to a Set of Circuit Equations Within a Given **Tolerance Criteria** & Specified **Iteration Loop Limitations**.
- The Designer Specifies a **Relative & Absolute Accuracy** for the Circuits Solution and the Simulator **Iteration Algorithm** Attempts to Converge onto a Solution that is within these Set Tolerance

● Error Messages for “NonConvergence” :

- “ **No Convergence in Operating Point (or DC Sweep)**”
- “ **Internal TimeStep is Too Small in Transient Analysis**”

● Possible Causes of “NonConvergence” :

- **Circuit Reasons** : (1). Incomplete Netlist; (2). Feedback; (3). Parasitics
- **Model Problems** : (1). Negative Conductance (2). Model Discontinuity
- **Simulation Options** : (1). Tolerances; (2). Iteration Algorithm



Accuracy Tolerances

- HSPICE uses Accuracy Tolerances specifications to help assure convergence by determining whether or not to exit the convergence loop.
- Absolute and relative accuracy tolerances:

Type	Option	Default
Nodel Voltage Tolerance	ABSV	50uV
	RELVDC	0.001(0.1%)
Current Element Tolerances	ABSI	1nA
	RELI	0.01(%)
	ABSMOS	1uA
	MELMOS	0.05(5%)

- ABSVDC&ABSI set the floor value below which values are ignored.
- Values above the floor use the relative tolerances of RELVDC & RELI.
- ABSMOS & RELMOS are the tolerances for MOSFET Drain Current.
- Number of iterations required is directly affected by accuracy setting.



AutoConvergence for DC Operating Point Analysis

● AutoConvergence Process:

- If Convergence is not Achieved in the Number of Iteration set by **ITL1**, HSPICE Initiates an **AutoConvergence Process**, in which it Manipulates **DCON**, **GRAMP**, and **GMINDC**, as well as **CONVERGENCE** in some Cases.
- **ITL1= x** : Set the **Maximum DC Iteration Limit**, **Default=100**.
Increasing Values as High as **400** Have Resulted in Convergence for Certain Large Circuits with **Feedback**, such as OP Amp & Sense Amplifiers.
- **GMINDC= x** : A Conductance that is Placed in Parallel with All PN Junction and All MOSFET Nodes for DC Analysis. It is Important in Stabilizing the Circuit During **DC Operating Point Analysis**.
- **CONVERGE=X** : INVOKES Different Methods for Solving NonConvergence Problems.
- **.OPTIONS OFF =:** turn off active device for easing DC calculation.



Steps for Solving DC Operating Point NonConvergence

● (1). Check Topology :

- Set **.OPTIONS NODE** to Get a **Nodes Cross Reference Listing** if You are in Doubt
- Check if All **PMOS Substrates** Connected to **VDD** or **Positive Supplies** ?
- Check if All **NMOS Substrates** Connected to **GND** or **Negative Supplies** ?
- Check if All **Vertical NPN Substrates** Connected to **GND** or **Negative Supplies** ?
- Check if All **Lateral PNP Substrates** Connected to **Negative Supplies** ?
- Check if All **Latches** Have Either an OFF Transistor or a **.NODESET** or an **.IC** on one side ?
- Check if All **Series Capacitors** Have a Parallel Resistance, or is **.OPTION DCSTEP** Set ?



Steps for Solving DC Operating Point NonConvergence (Cont.)

● (2). Check Your .MODEL Statements :

- Be Sure to Check your Model Parameter **Units**.
- Check if Your MOS Models had **Subshreshold** Parameter Set ? (**NFS=1e11** for HSPICE Level 1,2 &3 and **N0=1** for HSPICE BSIM1,2,3 Models & Level 28)
- Use MOS **ACM=1, ACM=2, or ACM=3** Source and Drain Diode Calculation to Automatically Generate **Parasitics**.

● (3). General Remarks :

- Circuits that Converge Individually and Fail when Combined are Almost Guaranteed to have a **Modeling** Problem.
- **Schmitt Triggers** are Unpredictable for DC Sweep and Sometimes for Operating Point for the same Reasons **Oscillators** and **Flip-Flops** are. Use **Slow Transient**.



Steps for Solving DC Operating Point NonConvergence (Cont.)

● (3). General Remarks (Cont.):

- **Open Loop OP Amp** have **High Gain**, which can Lead to Difficulties in Converging. ==> Start OP Amp in **Unity-Gain Configuration** and Open them Up in Transient Analysis with a **Voltage-Variable Resistor** or a **Resistor with a Large AC Value for AC Analysis**.

● (4). Check Your Options :

- **Remove** All Convergence-Related Options and Try First with No Special Options Setting.
- Check **NonConvergence Diagnostic Table** for NonConvergence Nodes. Look up NonConvergence Nodes in the Circuit Schematic. They are Generally **Latches**, **Schmitt Triggers** or **Oscillating** Nodes.
- **SCALE** and **SCALM** Scaling Options Have a Significant Effect on the Element and Model Parameters Values. **Be Careful with Units**.



Solutions for Some Typical NonConvergence Circuits

● Poor Initial Conditions :

- **Multistable Circuits** Need State Information to Guide the DC Solution. For Example, You must Initialize **Ring Oscillator** or **Flip-Flops** Circuits Using the **.IC** Statement.

● Inappropriate Model Parameters :

- It is Possible to Create a **Discontinuous** Ids or Capacitance Model by Imposing Nonphysical Model Parameters
- **Discontinuities** Most Exits at the Intersection of the **Linear** & **Saturation** Regions

● PN Junctions (Diodes, MOSFETs, BJTs) :

- **PN Junctions** Found in Diodes, BJTs, and MOSFET Models can Exhibit NonConvergence Behavior in Both DC and Transient Analysis.==> Options **GMINDC** and **GMIN** Automatically Parallel Every PN Junction with a Conductance.



Solutions for Some Typical NonConvergence Circuits (Cont.)

● Rapid Transitions in DC Sweep :

- Increase the **ITL2** , which is the Number for Iteration Allowed at Each Steps in DC Sweep Analysis, Value to 100, 200 or more. **Default=50**. (ITL1 is for the Initial Operating Point)

● DC Options for High Power Circuits :

- For **High Power Bipolar** Transistors, Set Options **ABSI** up from Default **1 nA** to Perhaps **10 mA**. Also, Minimum Voltage Tolerance Should be Raised from **50 uV** to **10mV**.
- If the Accuracy Given by Tight Tolerance is Necessary, Be Sure to Increase Option **ILT1** to **300~~400**.

● DC Options for Op Amp and Comparator :

- **High Gain Op Amp and Comparator** can Cause Convergence Problems, as well as Possible Violations of KCL Law. It is Sometimes Necessary to Tighten the Options **RELI** to **0.005** and **ABSI** to **1 pA**



Speed, Accuracy and Convergence for Tran analysis

■ simulation **Speed:**

- **.option fast** : set additional options to increase simulation speed with little loss of accuracy.
- **.option autostop**: terminates the simulation when all .measure statements have completed.

■ Simulation **Accuracy:**

- The **control options** and their default settings to Maximize accuracy are:

DVDT=4 LVLTIM=1 RMAX=5 SLOPETOL=0.75

FT=FS=0.25 BYPASS=1 BYTOL=MBYPASS*VNTOL=0.10M



Speed, Accuracy and Convergence for Tran analysis (cont.)

■ Timestep control for accuracy:

- **DVDT** control option selects the timestep control algorithm.
- **DELMAX** specifies the maximum allowed timestep size. For circuits contain oscillators or ideal delay elements, DELMAX should be set to one-hundredth of the period or less.
- **ACCURATE** control option tightens the simulation options to give the most accurate set of simulation algorithms and tolerances.

■ Models and accuracy:

- MOS Model parameter **ACM** that calculate defaults for **source & drain** junction parasitics.
- MOS Model parameter **CAPOP=4** that models the most advanced charge conservation.non-reciprocal gate capacitance.



Guidelines for choosing accuracy options

- Use the **ACCURATE** option for :
 - **Analog** or mixed signal circuits
 - Circuits with **long time constants**, such as rc networks
 - Circuits with **ground bounce**
- Use the default options (**DVDT=4**) for:
 - **Digital** circuits
 - **Digital cell** characterization
 - Circuits with fast moving edges (**short rise and fall times**)
- use ideal delay elements, use one of the following:
 - ACCURATE
 - DVDT=3
 - DVDT=4 and set DELMAX to a value small than the minimum pulse width if the minimum pulse width of any signal is less than the Mim. Ideal Delay



Numerical Integration Algorithm Controls

● Types of Numerical Integration Methods :

- Trapezoidal Algorithm (Default in HSPICE)

```
.OPTION METHOD = TRAP
```

- GEAR Algorithm

```
.OPTION METHOD = GEAR
```

● Trapezoidal Algorithm :

- Highest Accuracy
- Lowest Simulation Time
- Best for CMOS Digital Circuits

● GEAR Algorithm :

- Most Stable
- Highly Analog, Fast Moving Edges

● One Limitation of Trapezoidal Algorithm :

- It can Results in Unexpected Computational **Oscillation**. (Also Produces an Usually Long Simulation Time)
- For Circuits are Inductive in Nature, such as **Switching Regulator**, Use **GEAR** Algorithm. (**Circuit NonConvergent with TRAP will often Converge with GEAR**)



Timestep control algorithm

- **Dynamic timestep control algorithm:**

- Dynamically changing timestep **increase the accuracy** of simulation and **reduced the simulation time** by varying the value of the timestep over the transient analysis sweep depending upon the stability of the output.

- **Operation principles of Dynamic Timestep Control Algorithm:**

- decrease the Timestep value when nodal voltage are **changing quickly**.
- Increase the Timestep value when internal nodal voltage are **Stable**.

- **Selection of Timestep Control algorithm:**

- LVLTIM= 1 (default) uses the **DVDT** timestep algorithm.
- LVLTIM=2 LVLTIM = 2 uses the timestep algorithm for **local truncation error**.
- LVLTIM=3 uses the **DVDT timestep** algorithm with timestep reversal.
- To use the **GEAR** method of numerical integration and linearization, select **LVLTIM = 2**.
- To use the **TRAP** linearization algorithm, select LVLTIM = 1 or 3. Using LVLTIM = 1 (DVDT option) is the default, and helps **avoid internal timestep too small non-convergence**.



Timestep Control Algorithms

● Types of Dynamic Timestep Control Algorithm :

■ Iteration Count (Simplest):

- If Iterations Required to Converge $> \text{MAX}$, Decrease the Timestep
- If Iterations Required to Converge $< \text{MIN}$, Increase the Timestep

■ Local Truncation Error (LTE) :

- Use a Taylor Series Approximation to Calculate Next Timestep
- Timestep is Reduced if Actual Error is $>$ Predicted Error

■ DVDT (default):

- Based on the rate of change of nodal voltages


● Timestep Control Algorithm vs. Numerical Integration Algorithm :

- For **GEAR** is Selected \Rightarrow Defaults to **Truncation** Timestep Algorithm;
For **TRAP** is Selected \Rightarrow Defaults to **DVDT** Algorithm




Lab6 RLC circuit test

.option accuracy

 

Reduce maximum timestep

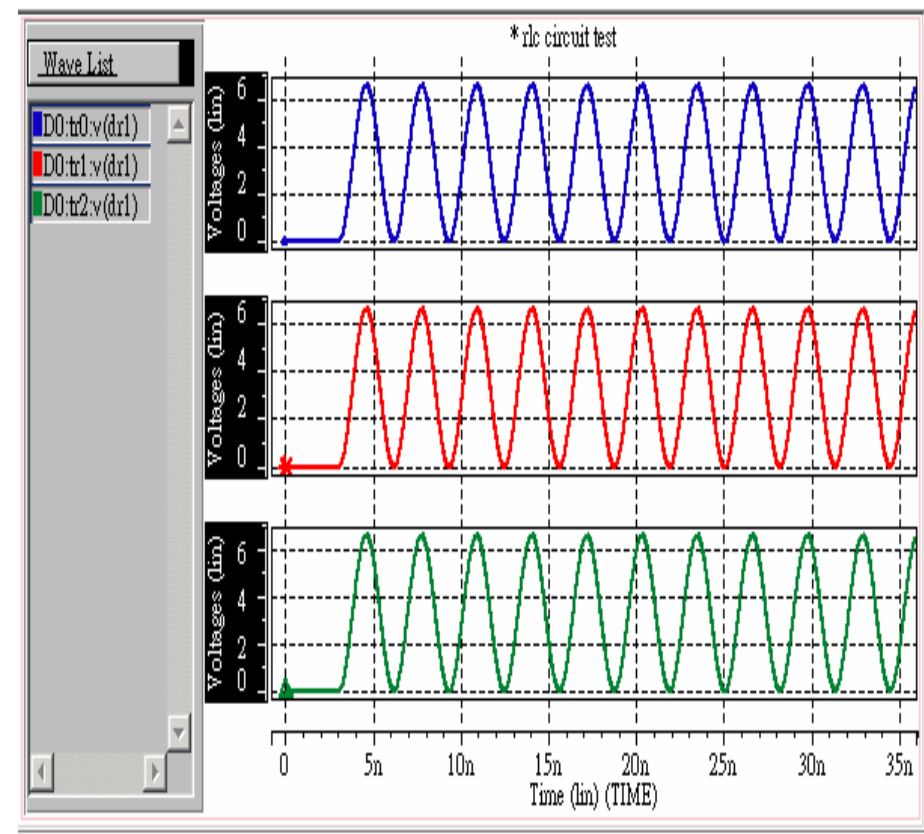



CHAPTER 9


Optimization & Statistical Analysis



Optimization

● Circuit Level Goal Optimization:

 - A procedure for **automatic searching** instance parameters to meet design goal
- Can be applied for both **.DC** , **.AC** and **.TRAN** analysis
- Optimization implemented in SBTSPICE can optimize one goal
- Optimization implemented in HSPICE can optimize **multi-goal** circuit parameter/device model parameter
- The parameter **searching range** must differentiate the optimization goal





Optimization Preliminaries

- **Circuit Topology Including Elements and Models**
- **List of Element to be Optimized**
 - **Initial Guess**, Minimum, Maximum
- **.Measure Statements for Evaluating Results**
 - **Circuit Performance Goals**
 - **Selection of Independent or Dependent Variables Measurement Region**
- **Specify Optimizer Model**



Optimization Syntax : General Form

■ Variable Parameters and Components :

```
.PARAM parameter = OPTxxx (init, min, max)
```

■ Optimizer Model Statement :

```
.MODEL method_name OPT <Parameter = val .....>
```

■ Analysis Statement Syntax :

```
.DC/AC/TRAN .....<DATA=filement > SWEEP OPTIMIZE = OPTxxx  
+ Results = meas_name MODEL = method_name
```

■ Measure Statement Syntax :

```
.MEASURE meas_name .....<GOAL=val> <MINVAL=val>
```



Example1

* rc network optimization

.ic 1 1

r1 1 0 rx

c1 1 0 cx

.model **opt1** opt

.option post

.param rx=**optrc**(.5,1e-2,1e+2)

+ cx=**optrc**(.5,1e-2,1e+2)

.tran .1 2 sweep optimize = **optrc** results = **trc,prc** model =**opt1**

.measure tran **trc** trig at=0 targ v(1) val=.3679 fall=1 goal =1s

.measure tran **prc** rms p(r1) goal=**50mw** ← Optimization goal by

.end

Specify parameter range

Analysis type and optimization algorithm



Optimization goal by measure command



Example1 (cont.)

Design target


- **1s** time constant
- **50mW** rms power dissipation through the resistor

 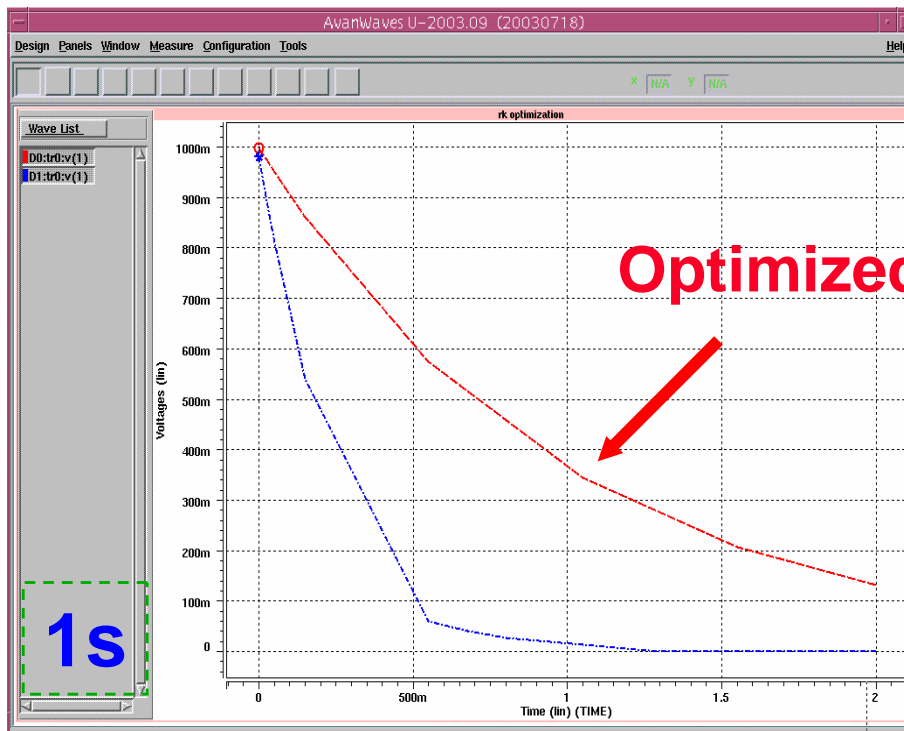



Example 2

Folded cascode OPAMP

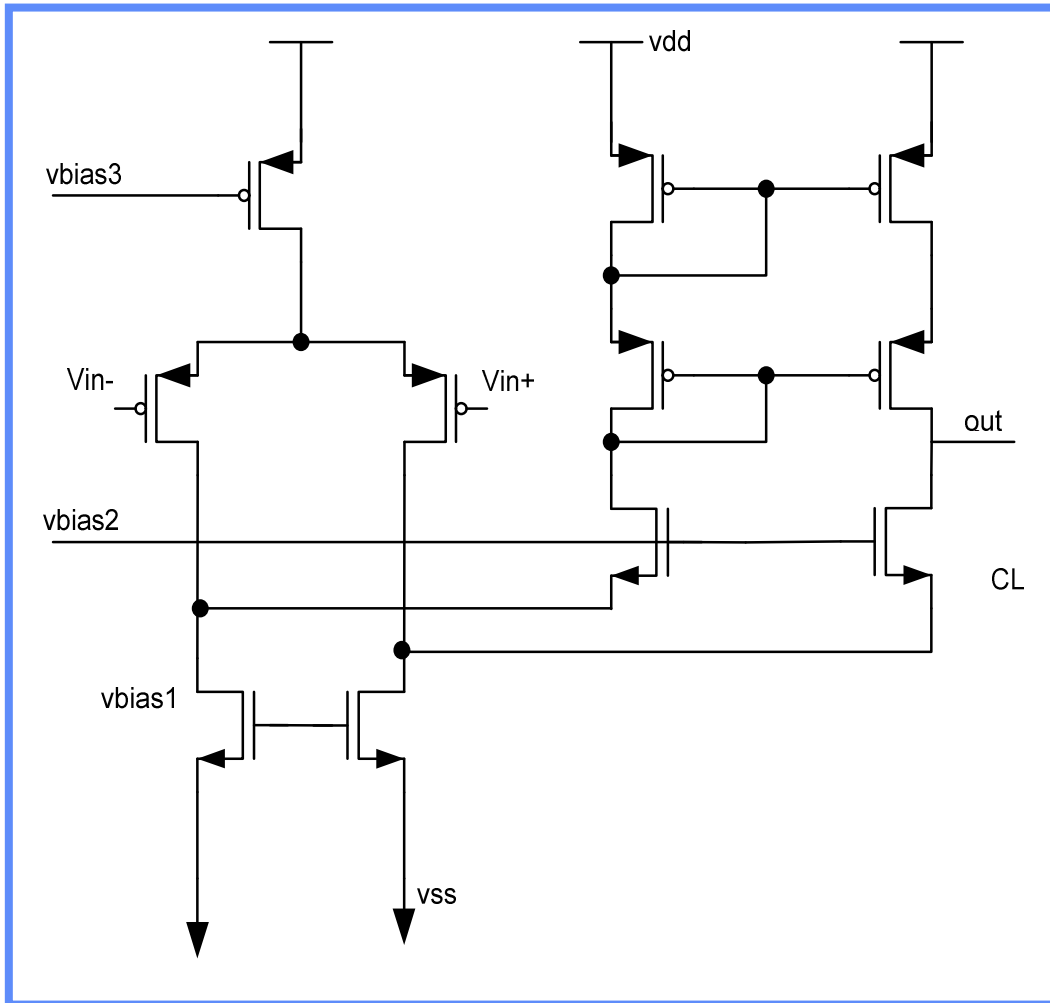

- * Target specification :
- * **CL = 1pF, Av>70dB,**
- * **GB=100MHz, PM>60**
- * **SR = 2 V/us, Pdiss < 10mW,**
- * with level2 process



Components & Models & Subckts

**** P CMOS folded-cascode opa**

**** COMPONENTS**

xopa ina inb out opa

*** Models & Subckts**

.protect

.lib 'mm0355v.l' TT

.unprotect

**** subcircuit operator amplifier**

.subckt opa va vb vout

**** differential amp**

M9 net3 net0 vdd! vdd! pch W=w1 L=1u

M1 net4 va net3 net3 pch W=w2 L=1u

M2 net5 vb net3 net3 pch W=w2 L=1u

M10 net4 net2 0 0 nch W=w3 L=1u

M11 net5 net2 0 0 nch W=w3 L=1u



Subckts

**** wide swing Cascode**

M3 net7 net6 vdd! vdd! pch W=w4 L=1u

M4 net6 net6 vdd! vdd! pch W=w4 L=1u

M5 net8 net8 net7 net7 pch W=w4 L=1u

M6 vout net8 net6 net6 pch W=w4 L=1u

M7 net8 net1 net5 0 nch W=w5 L=1u

M8 vout net1 net4 0 nch W=w5 L=1u

**** capacitor load**

Cl vout 0 1p

vbias1 net0 0 bias1

vbias2 net1 0 bias2

vbias3 net2 0 bias3

.ends



Sources & Controls

* Sources

```
.GLOBAL vdd! vss! vbias1 vbias2 vbias3
```

```
vdd vdd! 0 3.3
```

```
vss vss! 0 0
```

```
vr ina 0 dc 1.65
```

```
vin inb ina ac 1
```

** Controls

```
.op
```

```
.option post relv=1e-3 relvar=0.1 nomod acct post=2
```



Optimizations 1

*** OPTIMIZATION

**1 Variable Parameters and Components :*

```
.param bias1=opt1(2.4838,2.3,2.7)
```

```
+ bias2=opt1(1.543,1.3,1.8)
```

```
+ bias3=opt1(0.6852,0.5,1)
```

```
+ w1 =opt1(30u,5u,150u)
```

```
+ w2 =opt1(10u,2u,150u)
```

```
+ w3 =opt1(18u,1u,150u)
```

```
+ w4 =opt1(27u,1u,150u)
```

```
+ w5 =opt1(10u,1u,150u)
```

**2 Optimizer Model Statement :*

```
.model opt opt close=100 itropt=30
```



Optimizations 2

**3 Analysis Statement Syntax :*

```
.ac dec 10 1k 1000Meg sweep optimize=opt1 result =  
+ Amx,unity_gain_freq,phase_margin model=opt
```

**4 Measure Statement Syntax :*

```
.probe vdb(out) vp(out)
```

```
.meas Amx max vdb(out) goal = 70
```

```
.meas unity_gain_freq when vdb(out)=0 goal=230Meg
```

```
.meas ac phase_margin find=par'180+vp(out)' when  
+vdb(out)=0 goal=50
```

```
.end
```




Measure

```
$DATA1 SOURCE='HSPICE' VERSION='U-2003.09  '
.TITLE '** pmos folded-cascode opa'
index      bias1      bias2      bias3
           w1        w2        w3
           w4        w5        amx
unity_gain_freq phase_margin temper
alter#
28.0000    2.3200    1.8000    0.7785
           1.041e-04  9.773e-05  4.521e-05
           4.166e-05  5.313e-06  70.0928
           2.300e+08  50.0003   25.0000
           1.0000
```




Monte Carlo Analysis

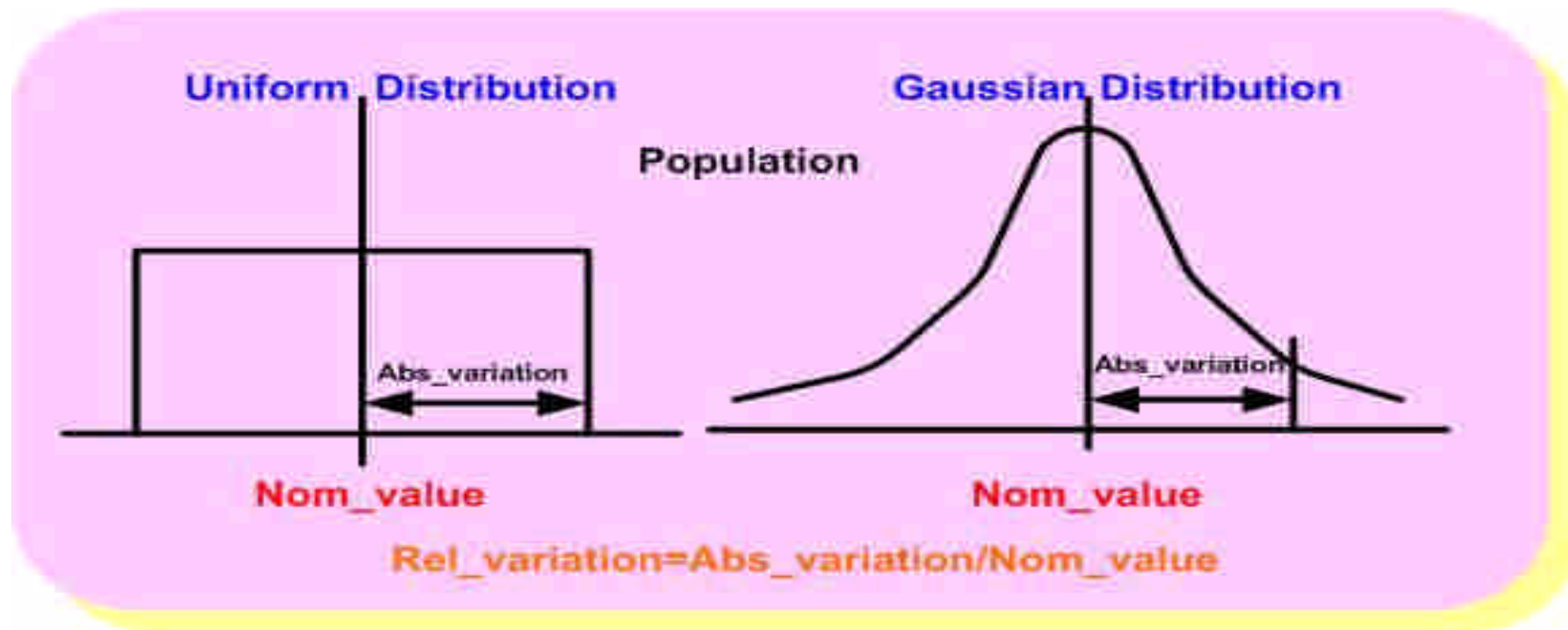- a random number generator
- **Gaussian** 、 **Uniform** 、 **Random Limit** Parameter Distribution
- **Relative** 、 **Absolute** 、 **Bimodal** 、 **min/max** variation variation



Monte Carlo Distribution



Monte Carlo Setup

◆ .PARAM statement

```
.PARAM xx=AUNIF(nominal_val, abs_variation <, multiplier>)  
.PARAM xx=UNIF(nominal_val, rel_variation <, multiplier>)  
.PARAM xx=GAUSS(nominal_val, rel_variation, sigma <, multiplier>)  
.PARAM xx=AGAUSS(nominal_val, abs_variation, sigma <, multiplier>)  
.PARAM xx=LIMIT(nominal_val, abs_variation)
```

where:

- **LIMIT Random limit distribution function** using absolute variation, +/- abs_variation is added to nominal_val based on whether the random outcome of a -1 to 1 distribution is greater or less than 0.
- **multiplier** If not specified, the default is 1. The calculation is repeated this many times and the largest deviation is saved.



Monte Carlo Setup(Cont.)

◆ .DC, .AC, or .TRAN analysis

■ Operating Point

```
.DC MONTE=val
```

■ DC Sweep

```
.DC vin 1 5 .25 SWEEP MONTE=val
```

■ AC Sweep

```
.AC dec 10 100 10meg SWEEP MONTE=val
```

■ TRAN Sweep


```
.TRAN 1n 10n SWEEP MONTE=val
```

val --> Monte Carlo iterations number



 
Example 1

```
mon1.sp  
.option list post=2  
.param rx=unif(1,.5) cx=unif(1,.5)  
*.param rx=unif(1,.5,10) cx=unif(1,.5,10)  
.tran .1 1 sweep monte=10  
.probe tran lv1(c1) lv2(r1)  
.ic 1 1  
r1 1 0 rx  
c1 1 0 cx  
.end
```





Example 1 (Cont.)

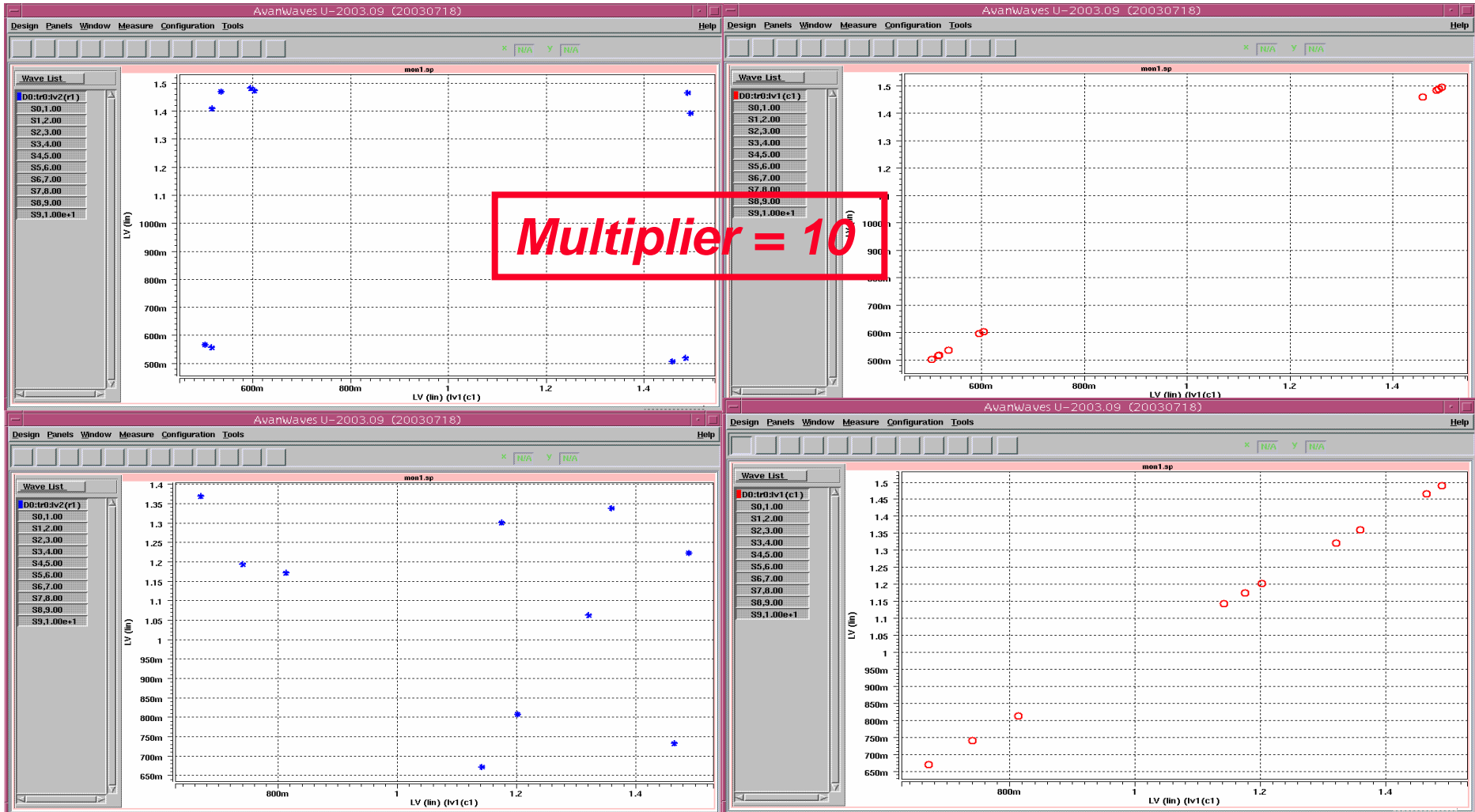



Example 2

Folded cascode OPAMP

```
vbias1 net0 0 2.32
```

```
vbias2 net1 0 1.8
```

```
vbias3 net2 0 0.778
```

*** Monte-carlo's parameter**

```
.param w1 =agauss(104.1u,1u,3)
```

```
+ w2 =agauss(97.73u,1u,3)
```

```
+ w3 =agauss(45.21u,1u,3)
```

```
+ w4 =agauss(41.67u,1u,3)
```

```
+ w5 =agauss(5.313u,1u,3)
```

*** Monte-Carlo Analysis**

```
.ac dec 10 1k 1000Meg sweep monte=10
```

*** Monte-Carlo measure**


```
.meas Amx max vdb(out)
```

```
.meas unity_gain_freq when vdb(out)=0
```


```
.meas ac phase_margin find=par'180+vp(out)' when vdb(out)=0
```



Example 2 (Cont.)

 

Monte-Carlo

 




CHAPTER 10

Applications Demonstration



Two-stage OP AMP Design

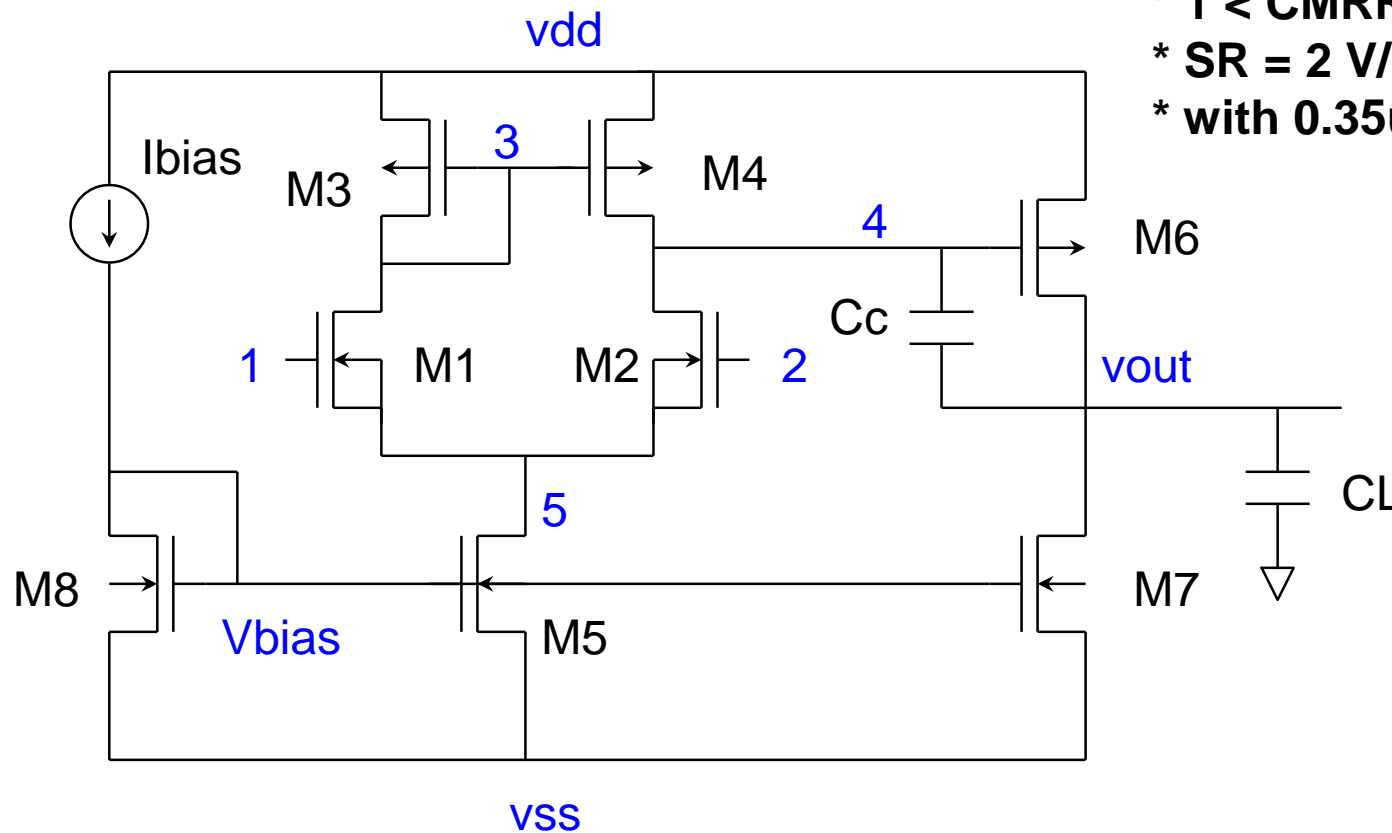- * Target specification :
- * $CL = 4\text{pF}$, $A_v > 4000$,
- * $GB = 2\text{MHz}$
- * $1 < CMRR < 4$, $0.8 < V_{out} < 4.2$
- * $SR = 2\text{ V/us}$, $P_{diss} < 10\text{mW}$,
- * with $0.35\mu\text{m}$ TSMC process





Netlist

***Two stage OP design**

.lib "mm0355v.l" mos_tt

.option post nomod

*** Netlist information**

M1 3 1 5 0 nch L=2u W=8u AS=18p AD=18p

+ PS=18u PD=18u

M2 4 2 5 0 nch L=2u W=8u AS=18p AD=18p

+ PS=18u PD=18u

M3 3 3 vdd vdd pch L=10u W=10u AS=12p AD=12p PS=16u PD=16u

M4 4 3 vdd vdd pch L=10u W=10u AS=12p AD=12p PS=16u PD=16u

M5 5 vbias vss vss nch L=2u W=7u AS=49p AD=49p PS=26u PD=26u

M6 vout 4 vdd vdd pch L=2u W=70u AS=490p AD=490p PS=150u PD=150u

M7 vout vbias vss vss nch L=2u W=130u AS=930p AD=930p

+ PS=260u PD=260u

M8 vbias vbias vss vss nch L=2u W=7u AS=49p AD=49p PS=26u PD=26u

*** Feedback CAP**

Cc vout 4 0.44pF

Cl vout 0 4pF

Ibias vdd vbias 8.8u

*** Voltage sources**

vdd vdd 0 5v

vss vss 0 0v




AC Frequency Analysis

```
vin2 2 0 2.5v  
vin1 1 0 DC 2.5v AC 1
```

```
*.OP
```
 
```
* AC Analysis function  
.ac dec 10 10 100MEG  
.probe ac vdb(vout)  
+ vp(vout) vdb(4) vp(4)  
.meas ac Unit_gain  
+ when vdb(vout)=0  
.meas ac phase_mar  
+ FIND vp(vout) when vdb(vout)=0
```







Transient Analysis : Slew Rate Analysis

* Transient analysis section
  
```
M1 3 vout 5 0 nch L=2u W=8u AS=18p AD=18p PS=18u PD=18u  
vin2 2 0 pulse(0v 5v 1n 1p 1p 600n 1200n)  
.tran 5n 2u  
.probe tran  
.save all
```





Future read

- [%~synopsys/sold/cur/doc/online/hspice/home.pdf](#)

HSPICE

HSPICE

HSPICE Simulation and Analysis User Guide

HSPICE Applications Manual

HSPICE Signal Integrity Guide

HSPICE Elements and Device Models Manual

HSPICE MOSFET Models Manual

HSPICE Command Reference

HSPICE Quick Reference Guide

HSPICE Device Models Quick Reference Guide

AVANWAVES

AvanWaves User Guide